


---

ECE-314, Fall 2008  
Signals and Systems

---

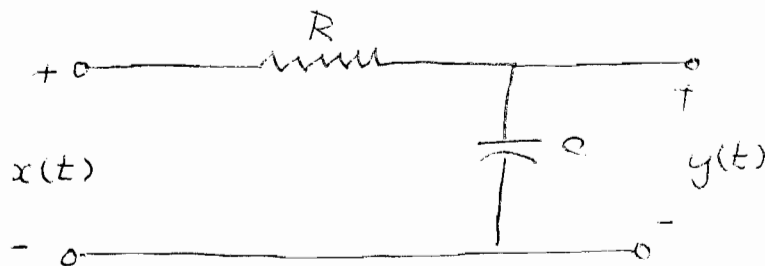Example: Stability & Causality

Consider the R-C circuit discussed before



$$x(t) = i(t)R + y(t)$$

$$x(t) = RC \frac{dy}{dt} + y(t)$$

Let us look at the response  $h(t)$  to a Dirac impulse at  $t=0$ , i.e.,  
 $h(t) = \mathcal{L}^{-1}(\delta(t))$  :

$$RC \frac{dh}{dt} + h(t) = \delta(t) \quad (1)$$

For  $t > 0_+$

$$RC \frac{dh}{dt} + h(t) = 0 \quad (2)$$

The solution to this DE can be obtained by substituting  $h(t) = e^{-\lambda t}$

$$RC(-\lambda e^{-\lambda t}) + e^{-\lambda t} = 0$$

$$\Rightarrow -\lambda RC + 1 = 0$$

$$\text{or } \lambda = 1/RC$$

The solution to the unforced system is of the form

$$h(t) = C_0 e^{-t/RC}$$

Heuristically speaking for the forced system the solution needs to be of the form:

$$h(t) = C_0 e^{-t/RC} u(t) \quad \left( \frac{du}{dt} = \delta(t) \right)$$

whence

$$h'(t) = -\frac{C_0}{RC} e^{-t/RC} u(t) + C_0 e^{-t/RC} \delta(t)$$

$$\text{or } h'(t) = -\frac{C_0}{RC} e^{-t/RC} u(t) + C_0 \delta(t)$$

$$RC h'(t) = -C_0 e^{-t/RC} u(t) + RC C_0 \delta(t)$$

$$+ h(t) = C_0 e^{-t/RC} u(t)$$

---


$$RC h'(t) + h(t) = RC C_0 \delta(t) = \delta(t) \text{ by (.)}$$

$$\Rightarrow C_0 = \frac{1}{RC}$$

- The impulse response of the R-C voltage divider circuit is :

$$h(t) = \frac{1}{RC} e^{-t/RC} u(t)$$

- Since  $h(t) = 0$ ,  $t < 0$ , the R-C voltage divider circuit is causal

- Also  $\int_0^{\infty} \frac{1}{RC} e^{-t/RC} dt = 1 < \infty$ ,

which means the R-C circuit is BIBO stable.

- This result is intuitive in that voltage division cannot result in a unbounded output and the maximum allowable gain out of voltage division is unity.