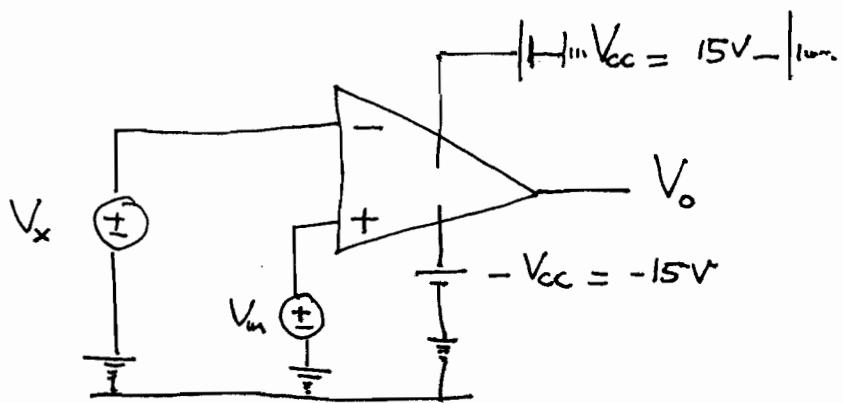



Operational Amplifier (Review)

Open Loop Mode :

Two inputs (V_+ & V_-)
One output

$$V_o = (V_{in} - V_x) A \quad A \text{ is open loop gain}$$

& very large $\approx 10^6$

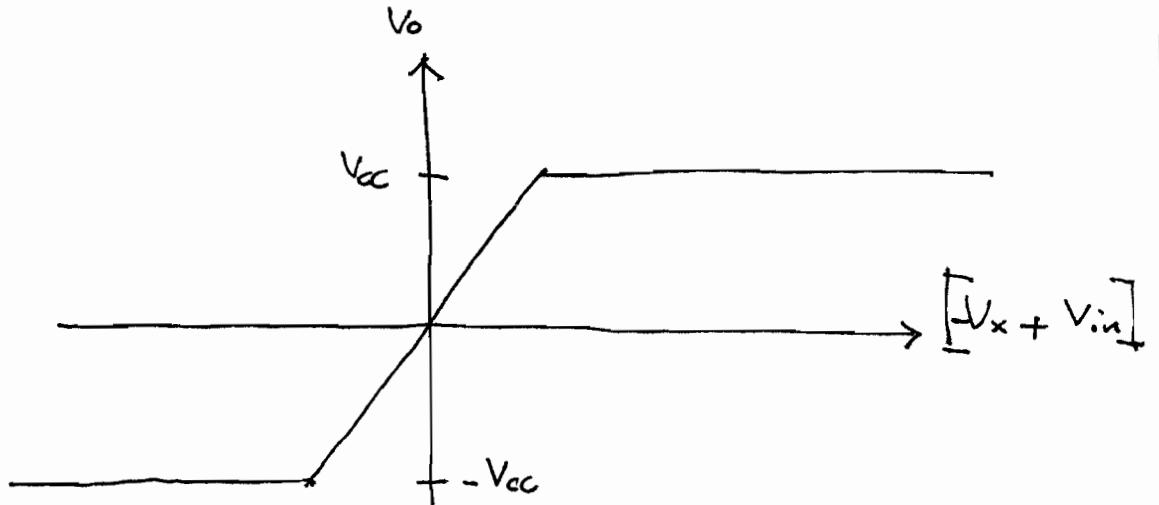


Linear Region $|V_x - V_{in}| < \frac{V_{cc}}{A}$

$$|V_x - V_{in}| < \text{few microvolts}$$

$$R_{in} = \infty$$

$$R_{out} = 0$$


Controlled Voltage Source Model

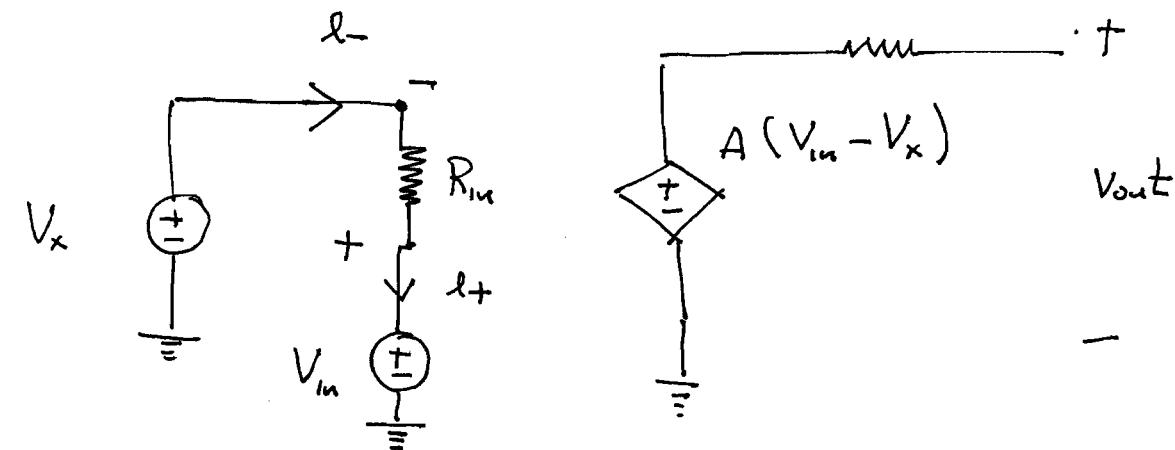


$$\text{If } i_+ = i_- = 0$$

$$R_{in} = \infty$$

Closed Loop Mode

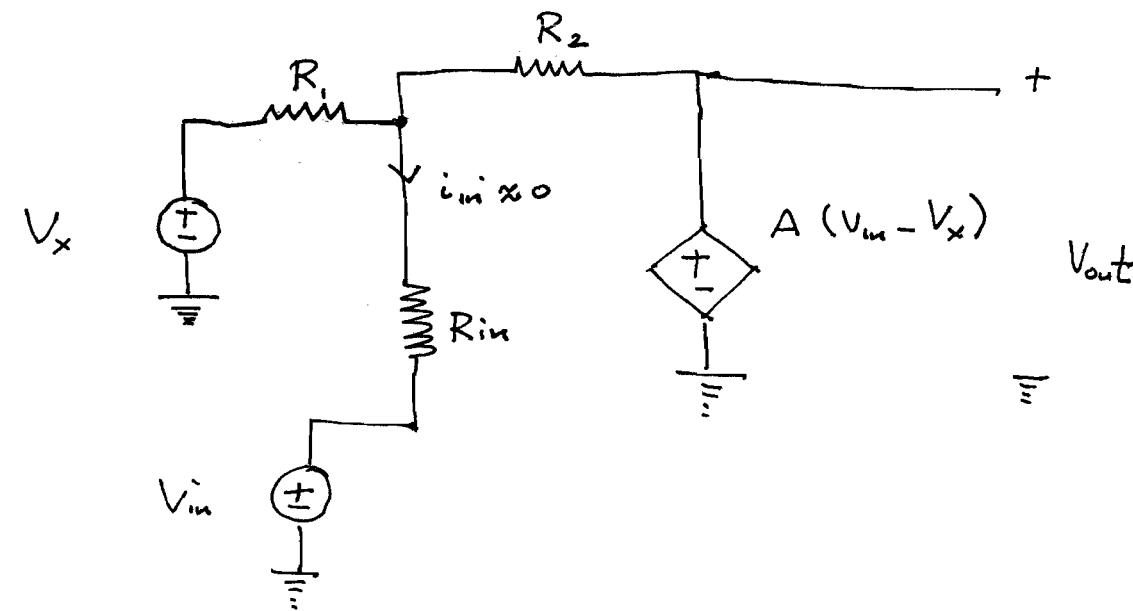

Non-Inverting Amplifier

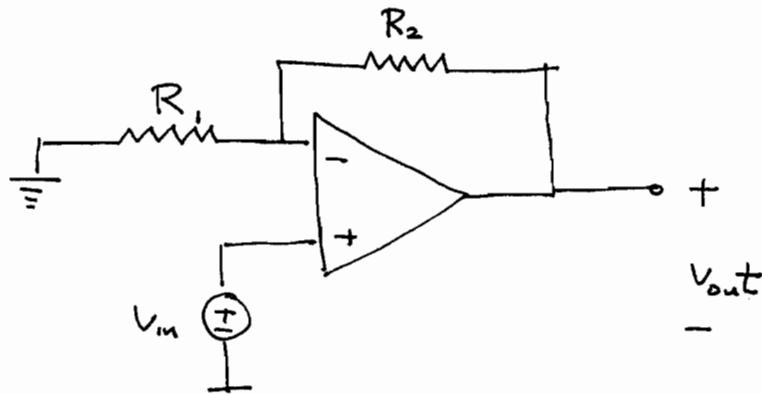


$$\frac{V_{out}(j\omega)}{R_2} - \cancel{V_-} + \frac{0 - \cancel{V_-}}{R_1} = 0$$

$$\frac{V_{out}(j\omega)}{R_2} = V_{in}(j\omega) \left[\frac{1}{R_2} + \frac{1}{R_1} \right]$$

$$\frac{V_{out}(j\omega)}{V_{in}(j\omega)} = \left(1 + \frac{R_2}{R_1} \right) = H(j\omega)$$

Inverting amplifier:

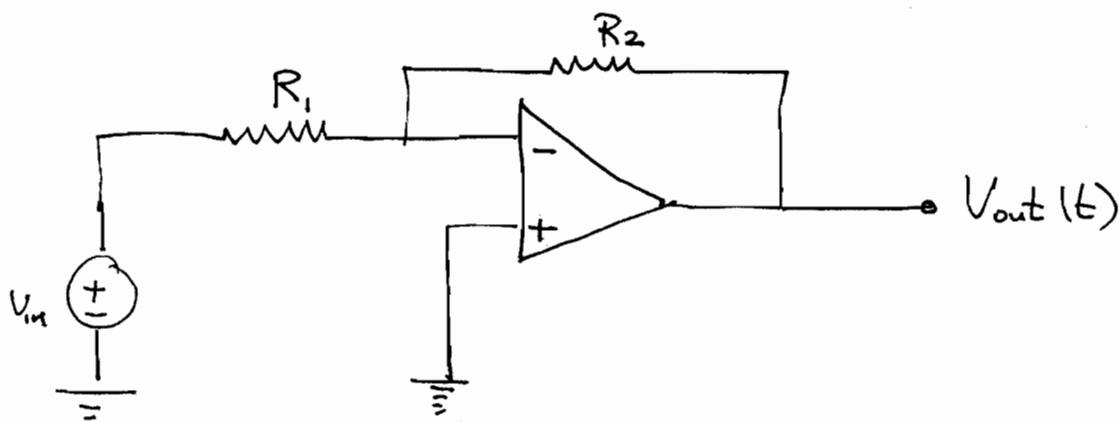


$$\frac{V_{out}(j\omega)}{R_2} - \cancel{V_-}^o + \frac{V_{in}(j\omega) - \cancel{V_-}^o}{R_1} = 0$$

$$\frac{V_{out}(j\omega)}{V_{in}(j\omega)} = -\frac{R_2}{R_1}$$

$$\Rightarrow \frac{V_{out}(t)}{V_{in}(t)} = -\frac{R_2}{R_1}$$

Voltage Follower:

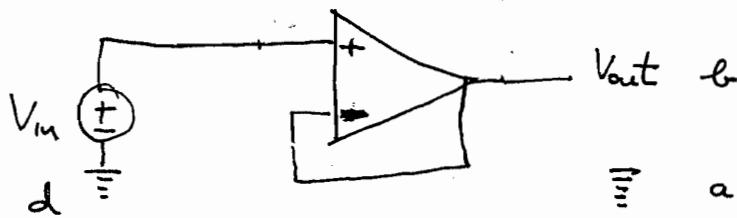

$$V_o = V_- = V_+ = V_{out}$$

$$V_{out}(t) - V_{in}(t) = 0$$


$$\Rightarrow V_{out}(t) = V_{in}(t) \quad [\text{Unity gain}]$$

Used to provide buffering between circuits

Different from just connecting wires

because $R_{in} = \infty$ & $R_{out} = 0$

Integrator or Differentiator:

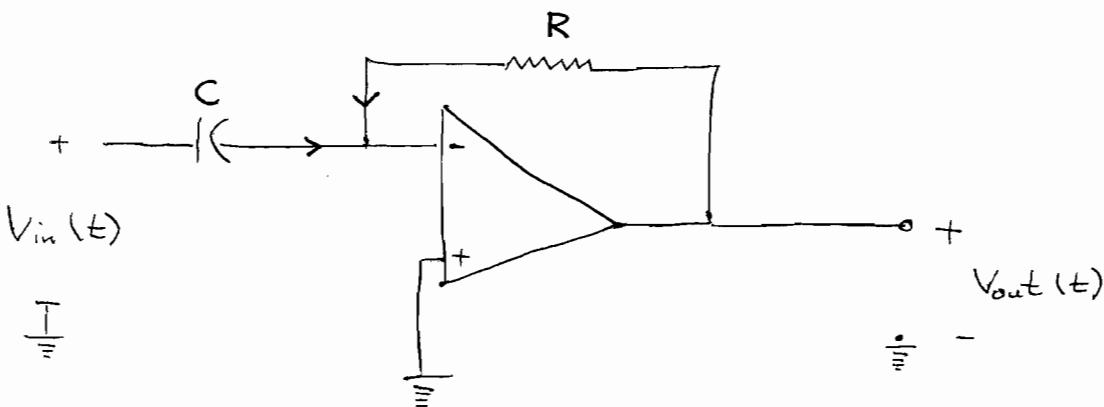



$$\frac{V_{out} - V_-}{R} + \frac{V_{in} - V_-}{\frac{1}{j\omega C}} = 0$$

$$\frac{V_{out}(j\omega)}{R} + j\omega C V_{in}(j\omega) = 0$$

$$\frac{V_{out}(j\omega)}{V_{in}(j\omega)} = H(j\omega) = -j\omega RC$$

$$20 \log_{10} (|H(j\omega)|) = 20 \log_{10} (\omega RC) \\ = 20 \log_{10} (\omega) + 20 \log_{10} (a)$$

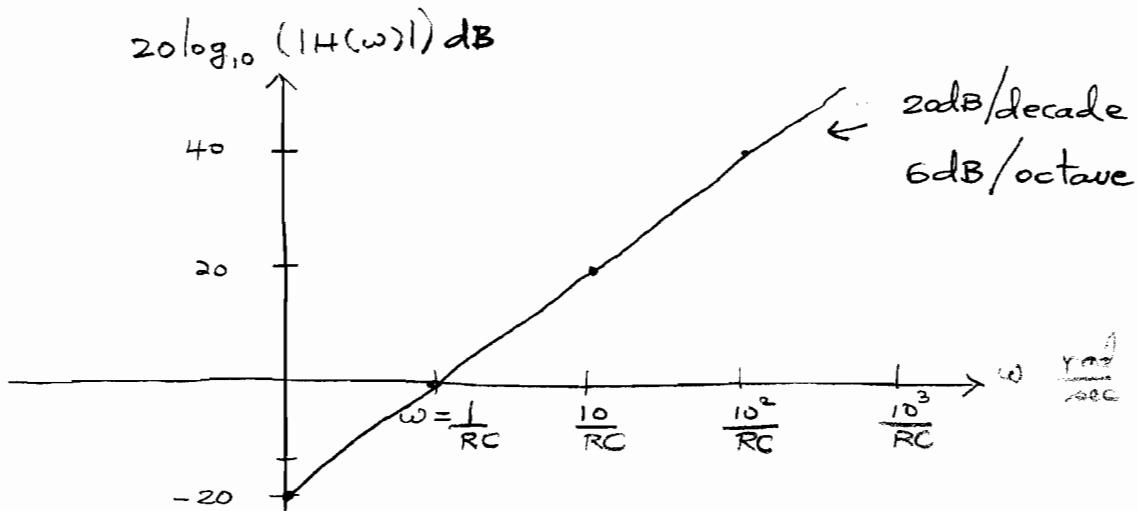

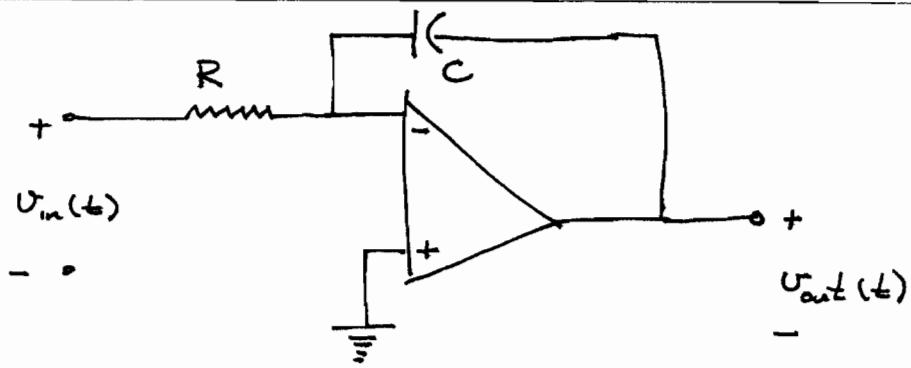


$$\frac{V_{out}(j\omega) - V_-}{\frac{1}{j\omega C}} + \frac{V_{in}(j\omega) - V_-}{R} = 0$$

$$j\omega C V_{out}(j\omega) = - \frac{V_{in}(j\omega)}{R}$$

$$H(j\omega) = \frac{V_{out}(j\omega)}{V_{in}(j\omega)} = - \frac{1}{j\omega RC}$$

$$20 \log_{10}(|H(j\omega)|) \text{ dB} = -20 \log_{10}(\omega RC)$$

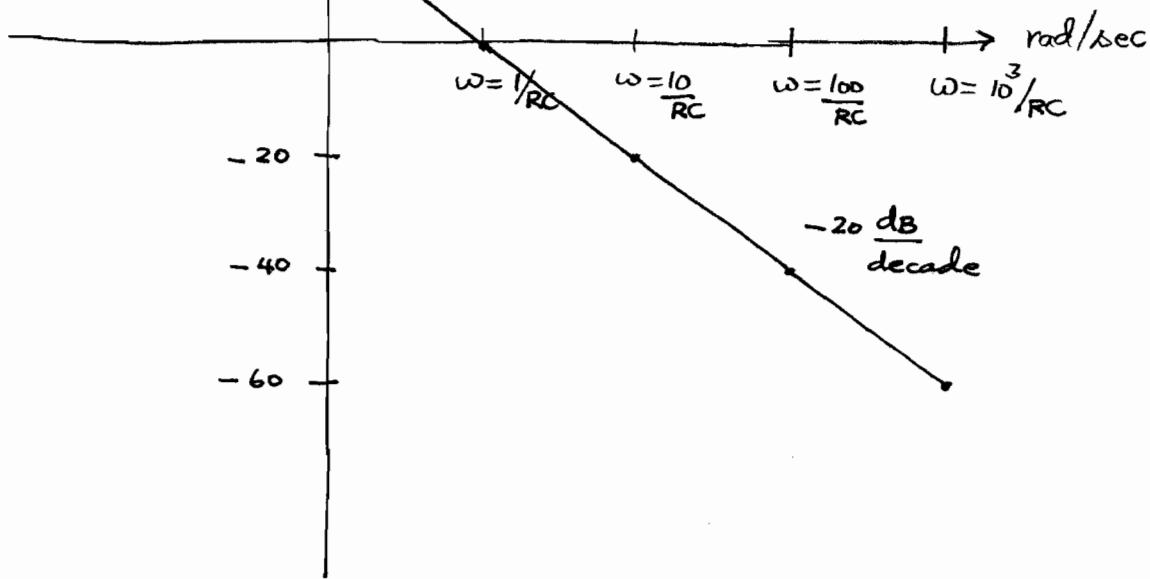

13-792
500 SHEETS FILLER 5 SQUARE
42-361 50 SHEETS EYE-EASE® 5 SQUARE
42-362 100 SHEETS EYE-EASE® 5 SQUARE
45-369 200 SHEETS EYE-EASE® 5 SQUARE
42-368 500 SHEETS EYE-EASE® 5 SQUARE
42-360 200 RECYCLED WHITE 5 SQUARE
42-358
Model = U.S.A.

