

LAB Assignment #4, for ECE 338

Assigned Sept 26th

Due Oct 1st

Description: Create a project with behavioral VHDL and evaluate the behavioral-to-hardware translation process.

Use Vivado to create a project. Add the following VHDL code which implements counters. Open 'elaborated design' and identify components of the schematic that correspond to elements of the VHDL code. Synthesize and open 'schematic', and identify components. Are there any significant differences? Please keep your lab report to 1 page, and include your name and the title "Lab #4: Behavioral-to-Schematic Translation, Counter". DO NOT EMAIL ANY LAB REPORTS. Print them out and give them to me in class.

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.NUMERIC_STD.ALL;

entity Counter is
    Port (
        clk: in std_logic;
        reset: in std_logic;
        ctrl: in std_logic_vector(3 downto 0);
        leds: out std_logic_vector(1 downto 0)
    );
end Counter;

architecture rtl of Counter is
    signal cnter1_reg, cnter1_next: unsigned(29 downto 0);
    signal cnter2_reg, cnter2_next: unsigned(29 downto 0);

begin

    process(clk, reset)
    begin
        if ( reset = '1' ) then
            cnter1_reg <= (others=>'0');
            cnter2_reg <= (others=>'0');
        elsif( rising_edge(clk) ) then
            cnter1_reg <= cnter1_next;
            cnter2_reg <= cnter2_next;
        end if;
    end process;

    -- Counter via conditional signal assignment
    cnter1_next <= cnter1_reg + 1 when ctrl(0) = '1' else
```

```

        cnter1_reg;

    leds(0) <= cnter1_reg(29) when ctrl(1) = '1' else
        '0';

    process (ctrl, cnter2_reg)
    begin
        leds(1) <= '0';
        cnter2_next <= cnter2_reg;

-- Counter via if assignment
        if ( ctrl(2) = '1' ) then
            cnter2_next <= cnter2_reg + 1;
        end if;

        if ( ctrl(3) = '1' ) then
            leds(1) <= cnter2_reg(29);
        end if;
    end process;
end rtl;

```

This lab is worth 10 points and requires a quick hardware demo.