

Synthesis of VHDL Code

This slide set covers

- Fundamental limitation of EDA software
- Realization of VHDL operator
- Realization of VHDL data type
- VHDL synthesis flow
- Timing consideration

Fundamental limitation of EDA software

Can *C-to-hardware* be done? No, not really

EDA tools consist of:

- Core: optimization algorithms
- Shell: wrappers around the **core** to carry out conversions, file operations, etc.

Theoretical computer science defines

- Computability (bounds on what algorithms can do)
- Computation complexity (inherent complexity to arrive at an optimal solution)

Computability and Computational Complexity

A problem is computable if an algorithm exists

Some problems are not computable, e.g., the **halting problem**

Can we develop a program that takes any program and its input, and determines whether the computation of that program will eventually halt?

Any attempt to examine the *meaning* of a program is uncomputable

For computable problems, analysis of computation complexity determines how fast an algorithm can run

Algorithms are analyzed for both *time* and *space* complexity

Computation time depends on the size of the input, the type of processor, programming language, compiler and even coding style

To eliminate the smaller factors, computational analysis focuses only on the **order** of the algorithm, as a function of the input size

Big-O notation

$f(n)$ is $O(g(n))$ if n_0 and c can be found to satisfy

$$f(n) < cg(n) \text{ for any } n, n > n_0$$

$g(n)$ is usually a simple function: 1, n , $\log_2 n$, n^2 , n^3 , 2^n

For example, the following are $O(n^2)$

$$(0.1n^2) \text{ <---> } (n^2 + 5n + 9) \text{ <---> } (500n^2 + 1000000)$$

Interpretation of Big-O

- Filter out constants and other less important terms
- Focus on *scaling factor* of an algorithm, i.e., what happens if the input size increases

input size	Big-O function						
	n	n	$\log_2 n$	$n \log_2 n$	n^2	n^3	2^n
2	2 μs	1 μs	2 μs	4 μs	8 μs	4 μs	
4	4 μs	2 μs	8 μs	16 μs	64 μs	16 μs	
8	8 μs	3 μs	24 μs	64 μs	512 μs	256 μs	
16	16 μs	4 μs	64 μs	256 μs	4 ms	66 ms	
32	32 μs	5 μs	160 μs	1 ms	33 ms	71 min	
48	48 μs	5.5 μs	268 μs	2 ms	111 ms	9 $year$	
64	64 μs	6 μs	384 μs	4 ms	262 ms	600,000 $year$	

Computation complexity

Intractable problems are algorithms with $O(2^n)$ -- not computable for large n

Frequently **tractable heuristic** algorithms exist, that run in polynomial time, but generate optimal solutions for only some inputs and/or generate *sub-optimal* solutions

Many problems encountered in synthesis are **intractable**

Synthesis software limitations

- Synthesis software cannot obtain the optimal solution
- Synthesis should be viewed as a transformation carried out using a **local search**
- Good VHDL code helps a lot by providing a good starting point for the local search

There are other design tasks that are intractable, and no amount of *fast hardware* or *clever heuristics* can be used to find the optimal solution

Therefore, it is impossible for EDA software to completely automate the design process

This limitation is **REAL** and is **HERE TO STAY!**

Realization of VHDL Operators

Logic operators: simple, direct mapping

Relational operators

=, /= fast, simple implementation exists

>, <, etc: more complex implementation, larger delay

Addition operator, and others that can be derived from addition including subtraction, negation and *abs*, has a multitude of implementations that trade-off speed and area

Even more complex than the relation operators

Synthesis support for other operators, e.g., shifting, multiplication, division, exponentiation, and floating point operations, is sporadic or non-existent

Because of their complexity, you must be extremely careful about using them in VHDL code

Realization of VHDL Operators

Operator with **two constant operands**: Simplified in preprocessing such that no hardware is inferred -- used because they clarify the code

```
constant OFFSET: integer := 8;
signal boundary: unsigned(8 downto 0);
signal overflow: std_logic;
overflow <= '1' when boundary > (2**OFFSET-1) else '0';
```

Operator with **one constant operand**: Can significantly reduce (cut-in-half) the hardware complexity, e.g., adder vs. incrementer, later implementable with half-adders

```
y <= rotate_right(x, y); -- full-fledged barrel shifter
y <= rotate_right(x, 3); -- rewiring, easy to implement
y <= x(2 downto 0) & x(7 downto 3); -- rewiring
```

Another example, 4-bit comparator: $x=y$ vs. $x=0$

$(x_3 \oplus y_3)' \cdot (x_2 \oplus y_2)' \cdot (x_1 \oplus y_1)' \cdot (x_0 \oplus y_0)'$ Full logic expression

$x'_3 \cdot x'_2 \cdot x'_1 \cdot x'_0$ Much easier, i.e., only a 4-input NOR gate

An Example 0.55 um Standard-Cell CMOS Implementation

width	VHDL operator									
	nand	xor	> _a	> _d	=	+1 _a	+1 _d	+ _a	+ _d	mux
area (gate count)										
8	8	22	25	68	26	27	33	51	118	21
16	16	44	52	102	51	55	73	101	265	42
32	32	85	105	211	102	113	153	203	437	85
64	64	171	212	398	204	227	313	405	755	171
delay (ns)										
8	0.1	0.4	4.0	1.9	1.0	2.4	1.5	4.2	3.2	0.3
16	0.1	0.4	8.6	3.7	1.7	5.5	3.3	8.2	5.5	0.3
32	0.1	0.4	17.6	6.7	1.8	11.6	7.5	16.2	11.1	0.3
64	0.1	0.4	35.7	14.3	2.2	24.0	15.7	32.2	22.9	0.3

a: optimized for area

d: optimized for delay

gate count: in equivalent 2-input NAND gates

Realization of VHDL data type


Use and synthesis of 'Z' and '-' (other values other than '0' and '1' not used in synthesis)

'Z' indicates *high impedance* (or open circuit)

Not a Boolean value but is exhibited in a physical circuit, e.g., as the output of a tri-state buffer

Tri-State Buffer

Tri-state buffer

 

oe: output enable

oe	y
0	Z
1	a_in

Major applications

- Bi-directional I/O pins
- Tri-state bus

VHDL description

```
y <= 'Z' when oe='1' else a_in;
```

'Z' cannot be used as input or manipulated

```
f <= 'Z' and a;
```


```
y <= data_a when in_bus='Z' else data_b;
```


Tri-State Buffer

Because a tri-state buffer is not an ordinary logic value, it is a good idea to separate it from regular code


Less clear (cannot be synthesized):

```
with sel select
  y <= 'Z' when "00",
      '1' when "01" | "11",
      '0' when others;
```

 


Better:

```
with sel select
  tmp <= '1' when "01" | "11",
        '0' when others;
  y <= 'Z' when sel="00" else tmp;
```

 

Bi-directional I/O Pins

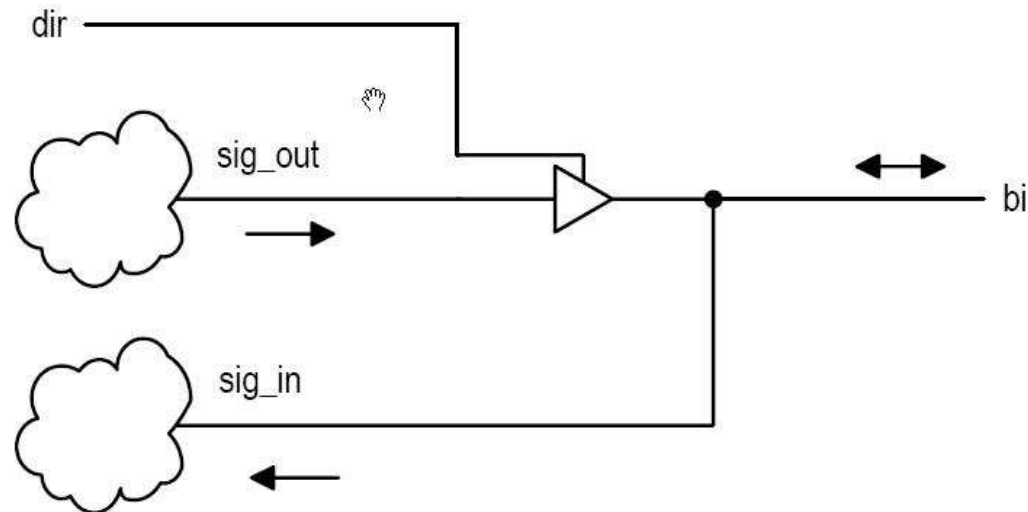
An important application of a tri-state buffer



```
entity bi_demo is  
  port (bi: inout std_logic;  
  ...  
begin  
  sig_out <= output_expression;  
  ...      <= expression_with_sig_in;  
  bi <= sig_out when dir = '1' else 'Z';  
  sig_in <= bi;
```


Bi-directional I/O Pins and Tri-State Bus
 
```
sig_in <= bi when dir = '0' else 'Z';
```



Alternative if driving *sig_in* with *sig_out* when *dir = '1'* is a problem

Tri-state bus

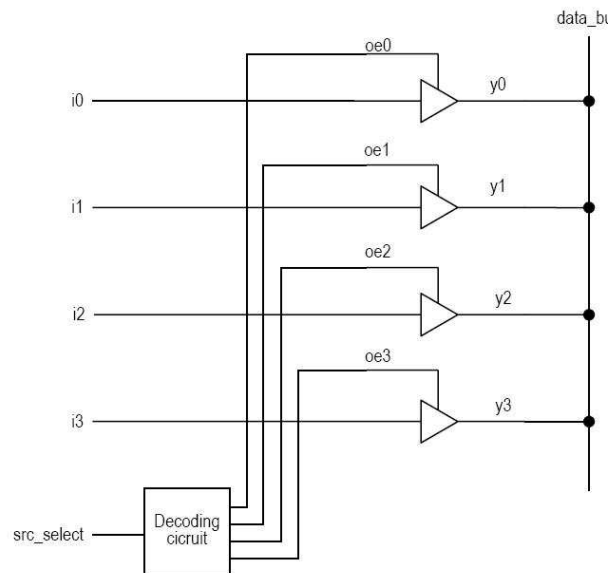

Tri-State Bus

```
with src_select select
    oe <= "0001" when "00",
        "0010" when "01",
        "0100" when "10",
        "1000" when others;

y0 <= i0 when oe(0)='1' else 'Z';
y1 <= i1 when oe(1)='1' else 'Z';
y2 <= i2 when oe(2)='1' else 'Z';
y3 <= i3 when oe(3)='1' else 'Z';

data_bus <= y0;
data_bus <= y1;
data_bus <= y2;
data_bus <= y3;
```

Problems with the tri-state bus

- Difficult to optimize, verify and test
- Somewhat difficult to design: is technology dependent and can result in 'contention'

Alternative to Tri-State Bus

Alternative to tri-state bus: **mux**

```
with src_select select
  data_bus <= i0 when "00",
             i1 when "01",
             i2 when "10",
             i3 when others;
```

Use of '-'

In conventional logic design, '-' used as input value: shorthand to make table compact

input req	output code	input req	output code
1 0 0	10	1 --	10
1 0 1	10	0 1 -	01
1 1 0	10	0 0 1	00
1 1 1	10	0 0 0	00
0 1 0	01		
0 1 1	01		
0 0 1	00		
0 0 0	00		

Use of '-'

'-' as output value: helps simplification, for example

- If '-' assigned to 0: $\bar{a}b + a\bar{b}$
- If '-' assigned to 1: $a + b$ (much less hardware than if 0)

input		output
<i>a</i>	<i>b</i>	<i>f</i>
0	0	0
0	1	1
1	0	1
1	1	-

As input value: (Syntactically correct but Wrong)

```
y <= "10" when req = "1--" else
    "01" when req = "01-" else
    "00" when req = "001" else
    "00"
```

Fix

```
y <= "10" when req(3) = '1' else
    "01" when req(3 downto 2) = "01" else
```

Use of '-'

```
"00" when req(3 downto 1) = "001" else
"00"
```

Another fix (must include 'use ieee.numeric_std.all):

```
y <= "10" when std_match(req, "1--") else
      "01" when std_match(req, "01-") else
      "00" when std_match(req, "001") else
      "00"
```

Wrong (but syntactically correct):

```
with req select
  y <= "10" when "1--",
      "01" when "01-",
      "00" when "001",
      "00" when others;
```

Fix:

```
with req select
  y <= "10" when "100" | "101" | "110" | "111",
      "01" when "010" | "011",
      "00" when others;
```

Use of '-'

'-' as an output value in VHDL may work with some software

```
sel <= a & b;
with sel select
    y <= '0' when "00",
        '1' when "01",
        '1' when "10",
        '-' when others;
```


VHDL Synthesis Flow

Synthesis: realize VHDL code using logic cells from the target device's library

Main steps:

- High-level synthesis (translates an algorithm into an architecture consisting of a *data path* and *control path* -- done by specialized hardware tools)
- RT level synthesis (the rest generate structural netlists)
- Logic synthesis
- Technology mapping

VHDL Synthesis Flow

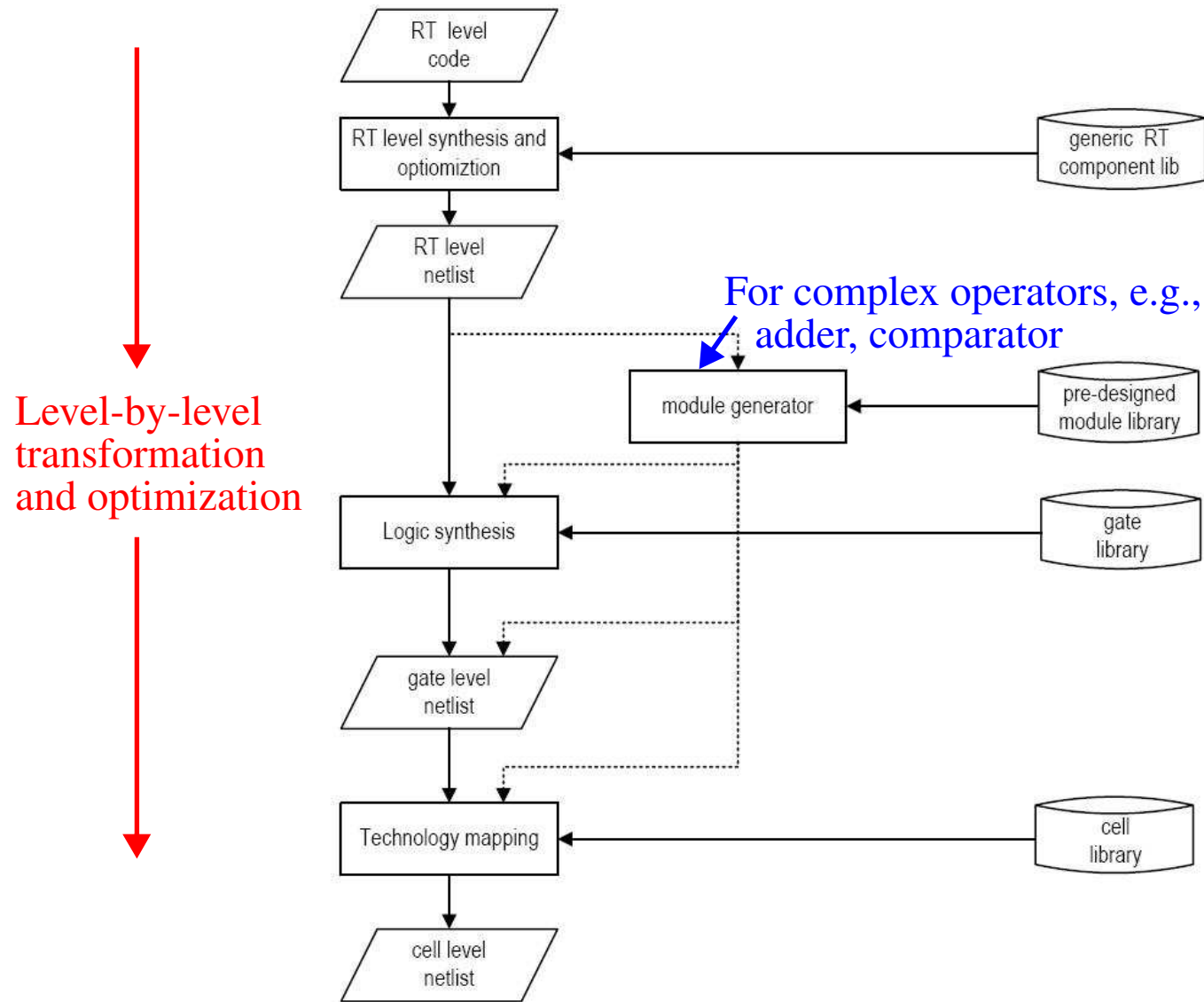

RT Level Synthesis

Realize VHDL code using *generic* RT-level components

Generic implies that the components are technology independent

Components classified into

- function units: those use to implement logic, relational and arith ops
- routing units: various MUXs to construct routing structure
- storage units: registers and latches

During RT-level synthesis, VHDL statements are converted to structural implementations (similar to derivation of the conceptual diagrams given earlier)

Some optimizations such as *operator sharing*, *common code elimination* and *constant propagation* can be applied to reduce hardware and improve performance

Unlike gate- and cell-level synthesis, optimizations are performed in an ad hoc way and scope is very limited

Good design can drastically alter the RT-level structure

Module Generator

The generic RT-level components (from RT-level synthesis) need to be transformed into lower-level components for further processing

Some components, such as logical operators and MUXs are simple and can be mapped directly into gate-level components

These are called **random logic** (low regularity) -- can be optimized later in logic synthesis

Other components such as an adder, subtracter, incrementer, comparator, shifter and multiplier are more complex and need a *module generator*

They usually show some kind of *repetitive structure*, and are called **regular logic**

Regular logic is usually designed in advance, as *presynthesized gate-* or *cell-level* netlists

Manual design can be more efficient than logic synthesis so these components are not flattened or optimized with other components during logic synthesis


Logic Synthesis

Implement the circuit with the optimal number of *generic* gate level components, such as NAND and NORs

The result is a structural view, expressed as Boolean functions

Logic synthesis can be divided into categories:

 - Two-level synthesis: sum-of-product format
- Multi-level synthesis (deals with large fan-ins, can trade-off area and speed)




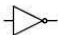



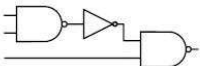

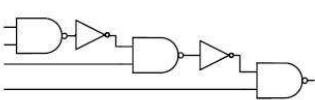

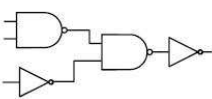

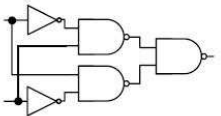
Multi-level synthesis is more efficient and flexible, but more difficult to carry out

Technology Mapping

Map *generic* gates to **device-dependent** logic cells

The technology library is provided by the vendors who manufactured, as in FPGAs, or will manufacture, as in ASICs, the device

Mapping in standard-cell ASIC


cell name (cost)	symbol	nand-not representation
not (2)		
nand2 (3)		
nand3 (4)		
nand4 (5)		
aci (4)		
xor (4)		

Technology mapping is a difficult process (intractable) and involves the use of *heuristics* and *rule-based* algorithms to find sub-optimal solutions


Std cell libraries usually contain several hundred cells, such as simple gates, 1-bit full adders, MUXs

The **nand-not** representation is used to facilitate the mapping process

Technology Mapping

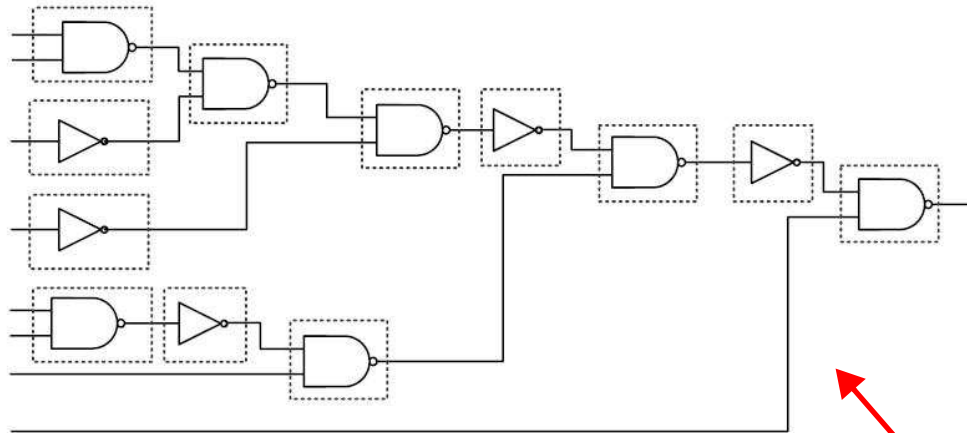

(a) Initial mapping

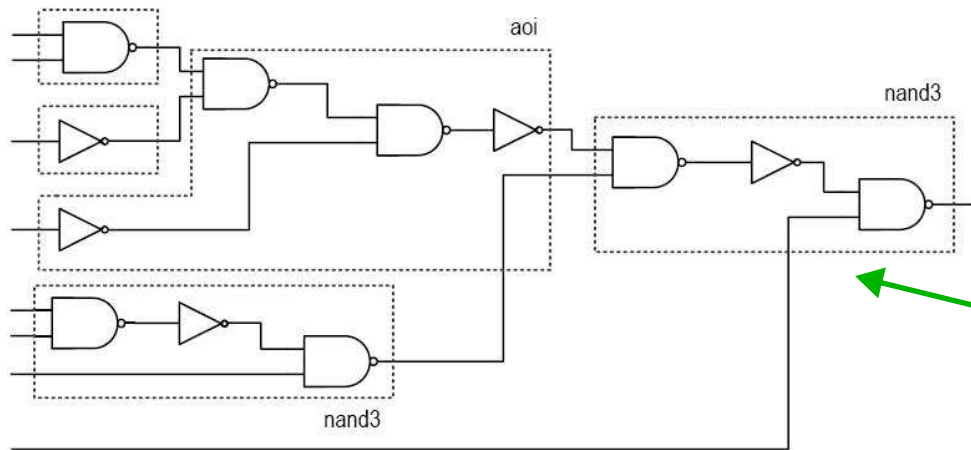

(b) Better mapping

Std cells are 'tuned' to a particular technology

They are manually designed at the transistor level


Multiple versions of the same function are common, each trading-off area and delay

Top design is a one-to-one, gate-to-cell mapping -- area is 31

Bottom design is optimized for area by selecting specific std cells from library -- result is 17


Technology Mapping

 Mapping into an FPGA (with 5-input LUT (Look-Up-Table) cells)



Direct mapping -- requires 4 LUTs

(a) Initial mapping

 

Optimized mapping -- requires 2 LUTs

(b) Better mapping

Effective Use of synthesis software


Logic operators: software can do a good job

Relational/Arith operators: manual intervention needed


Effective Use of Synthesis Software

"layout" and "routing structure":

 - Silicon chip is 2-dimensional square
- *rectangular* or *tree-shaped* circuit is easier to optimize



(a) Cascading-chain structure

 

Timing Considerations

Propagation delay

Synthesis with timing constraint

Hazards

Delay-sensitive design

Propagation Delay

Delay: time required to propagate a signal from an input port to a output port

Cell level delay (vs. RT-level) is the most accurate b/c netlist is final

Simplified model:


$$delay = d_{intrinsic} + rC_{load}$$

The $d_{intrinsic}$ term is the self-loading component, while the $r*C_{load}$ term is the driver's resistance and downstream capacitance components

Remember from basic circuit theory that *resistance*capacitance* = time (delay)

Propagation Delay

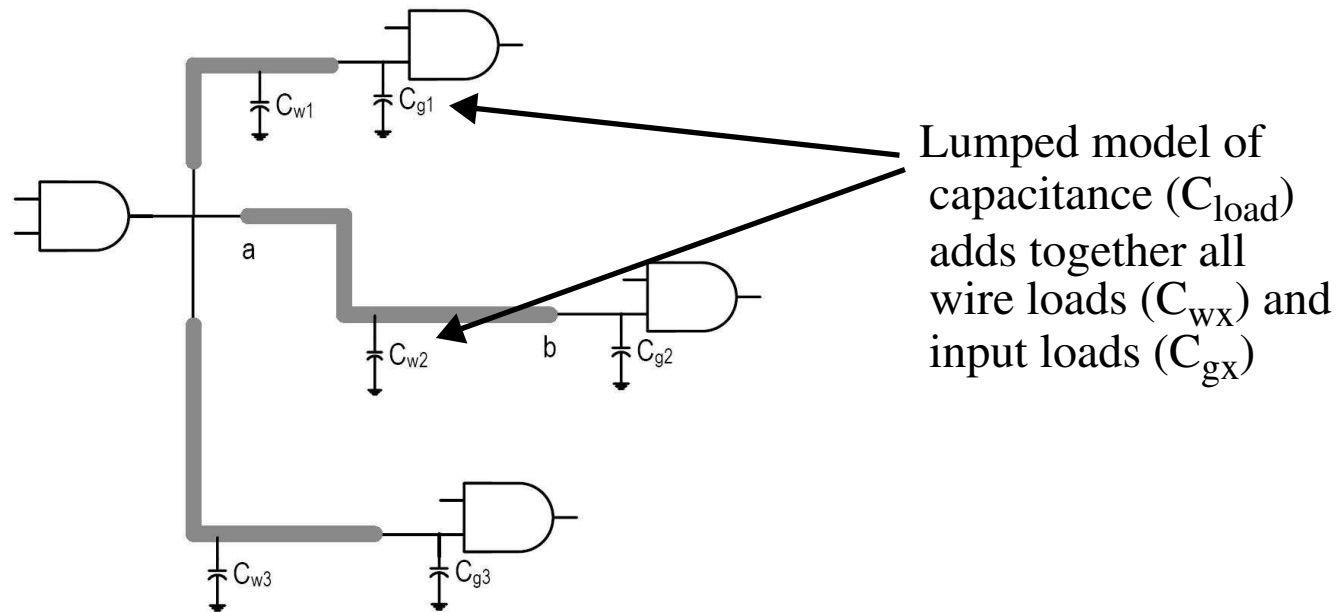The routing parasitics are not known at synthesis time, only after place and route



In advanced technologies, the impact of wire becomes more significant and must be considered to obtain an accurate delay estimation


System Delay

There are many paths between the inputs and outputs of a typical circuit

Each of them have different delays -- for overall system timing, we are interested in the **critical path** delay

System Delay


The worst **input-to-output** delay

 

Can be obtained from the netlist by treating it as a graph and extracting the longest path

Called the *topologically critical path*

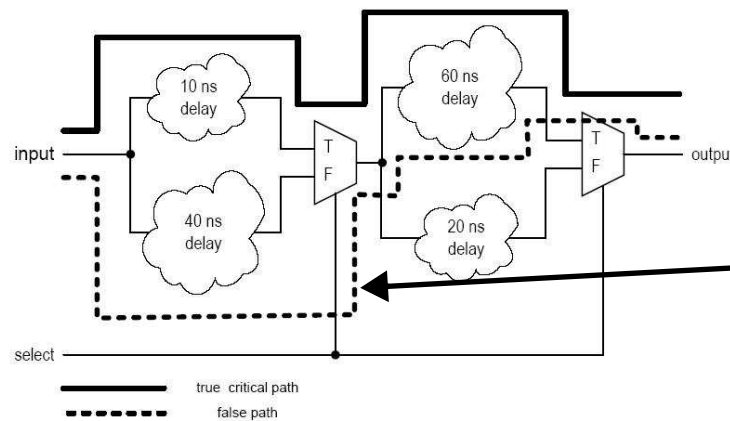This method has the drawback that the critical path obtained may be a **false path**



This critical path is a false path because MUXs don't allow it

That is, a path along which it is impossible to propagate a signal

System Delay


When estimating RT level delay:

- It is difficult if the design is mainly *random* logic because the simple logic will go through many transformations and optimizations
- However, if the design consists of many complex operators (such as addition) and function blocks, the critical path can be identified

This is true because these components are typically *pre-designed* and *optimized*

Synthesis with Timing Constraints

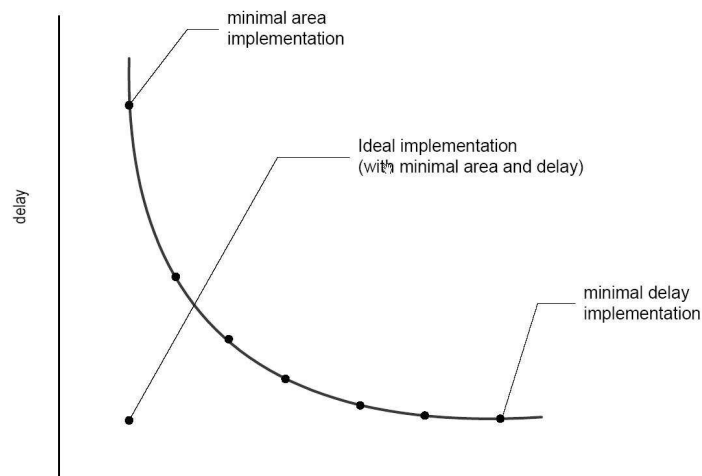
It is possible to reduce by delay at the expense of area, i.e., by adding extra logic




There are multiple implementations that trade-off area and delay

Synthesis with Timing Constraints

 Multilevel logic is flexible, making it possible to add additional gates to achieve shorter delay



(a) Optimized for area

 

(b) Optimized for delay

Timing constraints are sometimes needed to guarantee a specific performance metric


The synthesis process that considers timing constraints is carried out as follows

- Obtain the minimal-area implementation
- Identify the critical path
- Reduce the delay by adding extra logic
- Repeat 2 & 3 until meeting the constraint

Synthesis with Timing Constraints

It is also possible to perform this process at the RT level

 When the design consists of complex operators (blocks), *global* optimization can be explored (which is more efficient than synthesis optimization at the cell level)



Improvements can be made at the "architectural" level, which can have a huge impact on critical path delay and size


Timing Hazards

Propagation delay: time to obtain a stable output

Hazards: the fluctuation in the output occurring during the transient period

- Static hazard: glitch in output when the signal should be stable
- Dynamic hazard: a glitch in output during the transition

 
Hazards are caused by multiple converging paths of an output port



(a) Karnaugh map and schematic

$$sh = a\bar{b} + bc \quad (2\text{-to-}1 \text{ MUX})$$

Assume *a* and *c* are 1

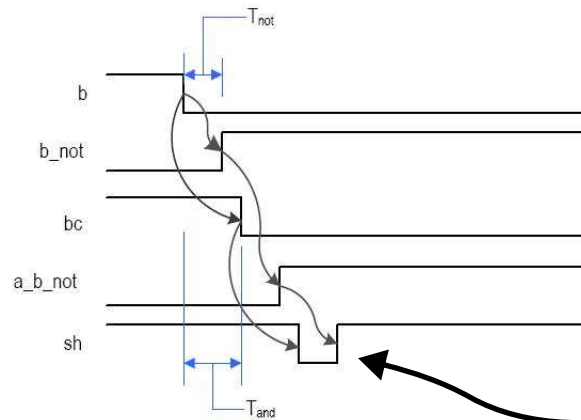


(b) Timing diagram


Static '0' hazard because of *extra* delay along *a_b_not* on transition of *b* from 1 to 0

Timing Hazards

Dynamic hazard

 

(a) Schematic

 



(b) Timing diagram

Assume $a = c = d = 1$

Transition of b from 1 to 0

Dealing with hazards

Some hazards can be eliminated in theory

  

Add an AND gate

(c) Revised Karnaugh map and schematic to eliminate hazards

Timing Hazards

Eliminating glitches is very difficult in reality, and almost impossible for synthesis

Multiple inputs can change simultaneously (e.g., cycling from 1111 -> 0000 in a counter)

How do we deal with them?

Ignore glitches in the transient period, e.g., sample after the signal is stabilized

Delay Sensitive Design and its Danger

Boolean algebra is the theoretical model for digital design and most algorithms used in the synthesis process


This model handles only stabilized signals (no transient behavior)

Delay-sensitive design, on the other hand, **depends** on the *transient behavior* (delay characteristics) of the circuit

Consider the addition of the *ac* (AND gate) to eliminate the static hazard -- the *ac* term is redundant UNTIL you consider the transient behavior

Delay Sensitive Design and its Danger

 Another circuit that depends on transient behavior is the *edge detection* circuit, with function $pulse = a \cdot \bar{a}$



Unfortunately, *synthesis* software does NOT consider transient behavior and will optimize and eliminate statements such as:

```
pulse <= a and (not a)
```

Other problems include

- During *technology mapping*, the gates specified may be re-mapped to other gates
- During *placement & routing*, wire delays may change creating unexpected results
- Difficult to test and verify (redundant logic is difficult to test for defects)

If *delay-sensitive design* is really needed, it should be done **manually**, not by synthesis