


Control

Control is the hard part of design.

The regularity found in arithmetic and memory structures usually not present in control structures.

Finite-State machines provide an organized structure for capturing control sequencing and operation.


Two types of state machines:

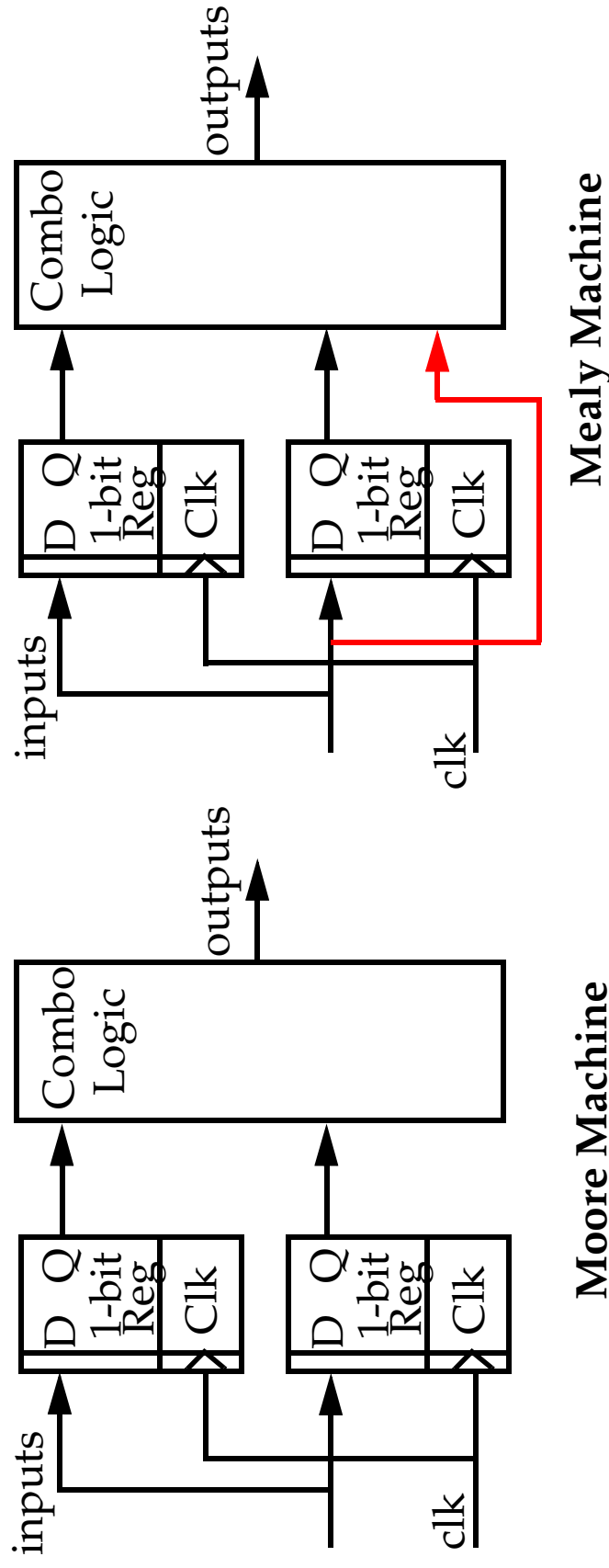

Control

State transition diagrams used to represent state machines.

Toll-booth controller example:

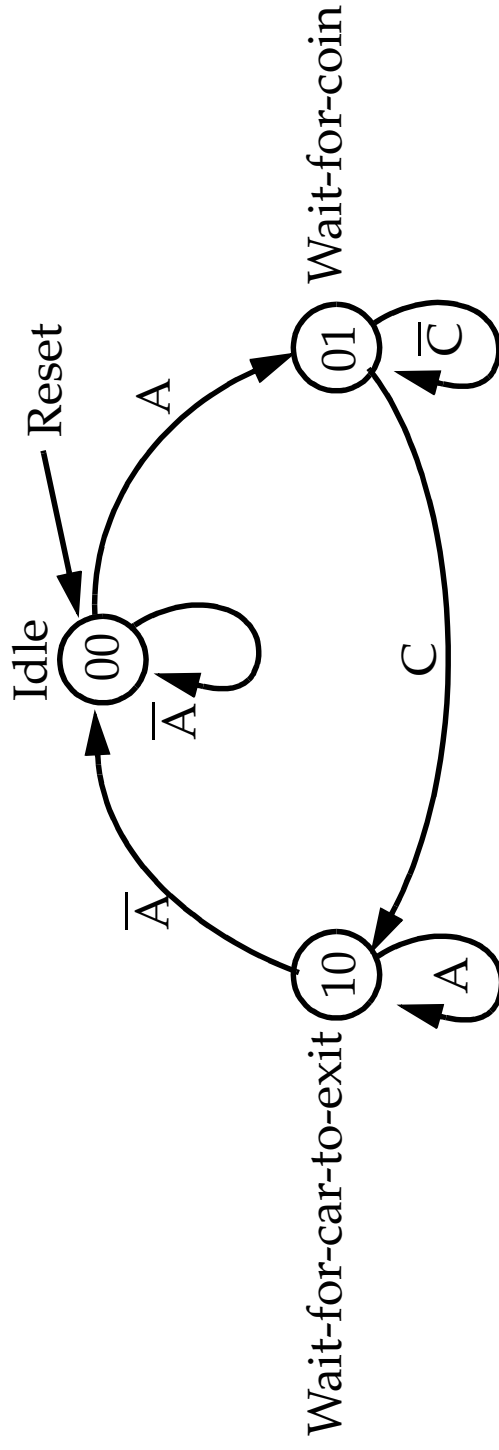

Inputs:

Reset

A (car in booth signal)

C (Change OK)

Outputs:

Turn green-light on

Write the state equations of the form:

if (state == oldstate & condition) next-state = newstate.

Rules for assigning state bits and output encoding method given in Weste and Eshraghian.

Control

Control logic in CMOS is constructed in two main ways:

- Two-level sum-of-products
- Multilevel logic

Two-level sum-of-products:

PLA implementation:

Regular structure for implementing combinational and sequential logic functions.

We have examined how to construct combinational functions already. Sequential functions (finite-state machines) implementations are identical except that outputs are fed back to the inputs via registers.

Pseudo n-MOS implementation main disadvantage is static power dissipation.

Dynamic CMOS implementation involves supplying the AND plane and OR plane with clocks (see Weste and Eshraghian).

Control

Multilevel Logic:

Most commonly used method for implementing control logic in CMOS.
Cascaded groups of regular gates such as INVERTERS, BUFFERS,
NANDs, NORs, XORs and AOIs.

CAD systems are highly effective at automatically minimizing the logic,
making state assignments and synthesizing layouts as gate-arrays or standard-cell layouts.

