

**University of New Mexico**  
Department of Electrical and Computer Engineering

---

**ECE 321 – Electronics I (Fall 2009)**

**Exam 3**

Name: Solution

Date: Nov. 18, 2009


Note: Only calculator, pencils, and pens are allowed.

1. (10 points) Fill in the blank:

- (a) In standard CMOS process, the source and drain are formed by using p<sup>+</sup> and n<sup>+</sup> layer masks.
- (b) The process of manufacturing transistors is called front-end and the process of manufacturing interconnects is called back-end.
- (c) CMP stands for Chemical Mechanical Polishing.
- (d) The effective width of two series NMOS with  $W_1=6\mu\text{m}$  and  $W_2=3\mu\text{m}$  is 2 $\mu\text{m}$ .
- (e) Electromigration is when metal lattice atoms swept out of position by current density

 2. (20 points) You are asked to layout the power and ground bus in the layout of a logic block in a real chip. Assume that the logic block draws 80mA of current and the metal thickness is 0.4  $\mu\text{m}$ . If the maximum current density  $J_{\text{max}} = 2 \times 10^6 \text{ A/cm}^2$ , determine the minimum width (in micron) of the interconnect that is needed to power the logic block.

$$J_{\text{max}} \times \text{Area} = \text{Current}$$
$$\text{Area} = \text{width} \times \text{thickness}$$



$$J_{\text{max}} = 2 \times 10^6 \text{ A/cm}^2 \times \left(\frac{100 \text{ cm}}{1 \text{ m}}\right)^2 \times \left(\frac{1 \text{ m}}{1 \times 10^6 \mu\text{m}}\right) = 0.02 \text{ A}/\mu\text{m}^2$$




$$0.02 \text{ A}/\mu\text{m}^2 = \frac{80 \times 10^{-3} \text{ A}}{w \times 0.4 \mu\text{m}} \Rightarrow w = 10 \mu\text{m}$$

3. (30 points) A three-input CMOS NAND gate is designed as shown below. Assume that  $V_{DD}=1.2$  V,  $K'_n=90 \mu\text{A}/\text{V}^2$ ,  $V_{tn}=0.4$  V,  $K'_p=50 \mu\text{A}/\text{V}^2$ , and  $V_{tp}=-0.5$  V in the 100nm technology node.

(a) Determine the width of NMOS and PMOS transistors in this NAND gate, such that the worst case delay becomes equivalent to a referenced inverter with  $W_n=1\mu\text{m}$  and  $W_p=2\mu\text{m}$ .

(b) For the device sizes found in part (a), determine the switching threshold voltage,  $V_M$ , when all inputs are tied together.

 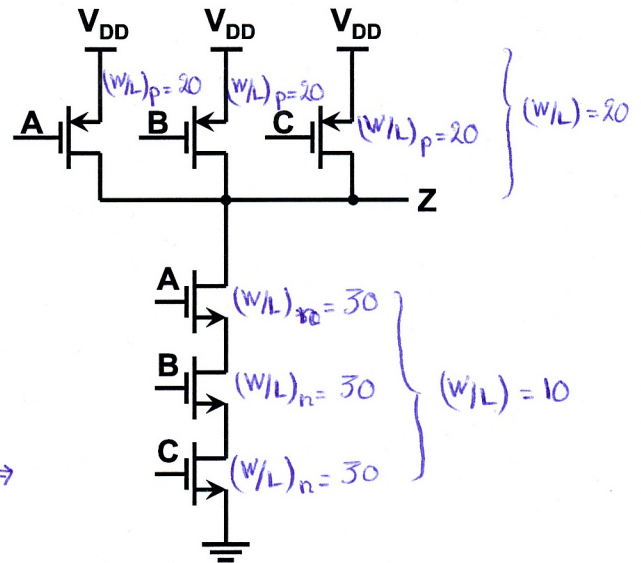 (c) Find the maximum  $I_{DD}$  current for this NAND gate.



$$I_p = I_n$$

$$\frac{K'_p}{2} (W/L)_p [V_{gs_p} - V_{tp}]^2 =$$

$$\frac{K'_n}{2} (W/L)_n [V_{gs_n} - V_{tn}]^2 \Rightarrow$$

$$\frac{50 \mu\text{A}/\text{V}^2}{2} \times 60 \times [(V_M - 1.2) - (-0.5)]^2 = \frac{90 \mu\text{A}/\text{V}^2}{2} \times 10 \times [V_M - 0.4]^2 \Rightarrow$$

$$V_M = 0.594 \text{ V}$$

c)

$$I_{DD, \max} = I_n(V_M) = \frac{90 \mu\text{A}/\text{V}^2}{2} (10) [0.594 - 0.4]^2 \Rightarrow I_{DD, \max} = 1.69 \times 10^{-5} \text{ A}$$


4. (40 points) We would like to design the following circuit such that the worst case propagation delays ( $t_{pHL}$  and  $t_{pLH}$ ) are limited to 2.14 ns. Use Elmore delay equation to determine the W/L for PMOS and NMOS used in the 3-input NAND gate. Assume that  $V_{DD}=1.2$  V,  $K'_n=90 \mu A/V^2$ ,  $V_{tn}=0.4$  V,  $K'_p=50 \mu A/V^2$ , and  $V_{tp}=-0.5$  V in the 100nm technology node. Also assume that the transistors stay in saturation region for the length of the transition.

$$t_{pLH} = 0.69 \tau \quad \text{where} \quad \tau = \sum_i R_i C_i$$

$$\tau = \frac{t_{pLH}}{0.69}$$

$$\tau = (R+10k) \times 100fF + (R+10k) \times (10fF+20fF+30fF) + (R+10k+1k) \times (10fF) + (R+10k+1k+1k) \times (20fF)$$
 
$$\tau = \frac{2.14}{0.69} \rightarrow R_{out} = 6.06 \text{ k}\Omega$$



$$t_{pHL} = 0.69 (R_{out}) C_L \rightarrow C_L = 0.512 \text{ pF}$$

$$I_{avg} ? \quad t_{pLH} = \frac{C_L \times (V_{dd}/2)}{I_{avg}} \rightarrow I_{avg} = 149.5 \mu A$$



$$I_{avg} = \frac{K'_n}{2} (W/L)_n (V_{dd} - V_{tn})^2 \rightarrow (W/L)_n = \frac{I_{avg}}{\frac{K'_n}{2} (V_{dd} - V_{tn})^2} = 4.98 \approx 5$$

$$(W/L)_p = \frac{I_{avg}}{\frac{K'_p}{2} (V_{dd} - |V_{tp}|)^2} \rightarrow (W/L)_p = 11.7 \approx 12 \Rightarrow$$

