

**University of New Mexico**  
Department of Electrical and Computer Engineering

---

**ECE 321 – Electronics I (Fall 2009)**

**Exam 4**


Name: \_\_\_\_\_

Date: Dec. 9, 2009


Note: Only calculator, pencils, and pens are allowed.

1. (10 points) Fill in the blank:
  - (a) In a flip-flop, the time that the input data needs to be stable after the rising edge of the clock is called \_\_\_\_\_.
  - (b) Contamination delay is \_\_\_\_\_.
  - (c) An 8-input dynamic logic NAND gate requires \_\_\_\_\_ transistors.
  - (d) NMOS is good in passing \_\_\_\_\_ and PMOS is good in passing \_\_\_\_\_.
  - (e) If the average propagation delay of an inverter is 100ps, then a ring oscillator of 21 stages of inverter will oscillate at the frequency of \_\_\_\_\_ MHz.
  
2. (20 points) Dynamic logic design problem:
  - (a) Draw the circuit diagram of a dynamic logic that performs  $Z = \overline{A + B(C + D)}$ .
  - (b) Determine the width of NMOS transistors, such that the worst case  $t_{pHL}$  delay becomes roughly equivalent to a referenced inverter with  $W_n=1\mu\text{m}$  and  $W_p=2\mu\text{m}$ .

 3. (30 points) Consider the following sequential circuit with 4 edge-triggered flip-flops and some logic gates. Assume that  $t_{SU} = 3 \text{ ns}$ ,  $t_{hold} = 2 \text{ ns}$ , and  $t_{C2Q} = 1 \text{ ns}$ .
- Identify the path with the maximum delay (critical path) on the schematic.
  - What is the maximum operating frequency of this circuit?
  - Identify the path with minimum delay on the schematic.
  - Does this circuit violate the hold time constraint? Why?



 4. (40 points) The following circuit is a 4-input dynamic logic.
- Identify the logic function for the output Z.
  - What input vector imposes the worst case charge sharing during the evaluation time?
  - Compute the final voltage at Z, if the input vector is ABCDE=11000 during evaluation after charge sharing. Assume that  $V_{th} = 0.4V$ .
  - Determine the width of the PMOS such that the maximum worst case pre-charge time delay (0 to 90%) is limited to 250ps. (The worst case is when all the inputs are at  $V_{DD}$  such that all the intermediate capacitors contribute to the delay). Assume that  $V_{DD} = 1.2 V$ ,  $K'_p = 50 \mu A/V^2$ , and  $V_{tp} = -0.5 V$  in the 100nm technology node. For simplicity assume that the PMOS will stay in saturation during the transition.



5. (10 bonus points) The following are bonus questions:
- (a) In problem 3, how do you modify the circuit to avoid the hold time violation without any penalty on the operating frequency? (5 bonus credit)
  - (b) Leakage current is another problem for dynamic logics. If  $I_{off}$  is 100pA for each NMOS in problem 4, which input vectors give the maximum leakage? How much is the maximum leakage? (5 bonus credit)