
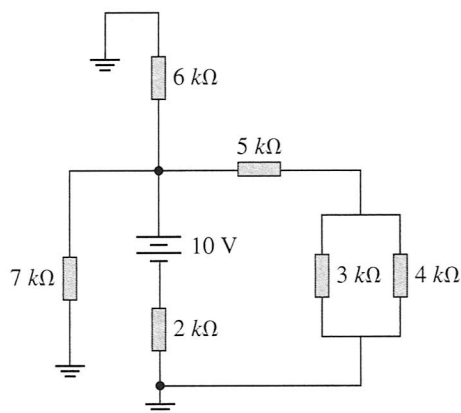


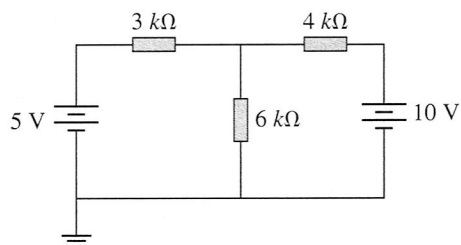- 1-21. Using analysis by inspection, write the expression for the voltage across the $2\text{ k}\Omega$ resistor and solve for its value.



Mixing Voltage and Current Divider Analysis

- 1-22. Find I_{6k} .




Hint: When we have two power supplies and a linear (resistive) network, we solve in three steps.

- (1) Set one power supply to 0 V and calculate current in the $6\text{ k}\Omega$ resistor from the nonzero power supply.
- (2) Reverse the power supply roles and recalculate I_{6k} .
- (3) The final answer is the sum of the two currents.


This is known as the superposition theorem and can be applied only for linear elements.

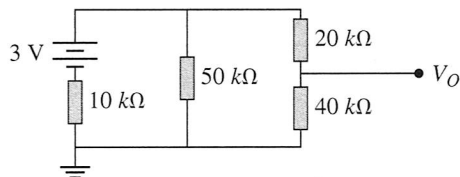- 1-23. Solve for V_O using a method of inspection (current divider, voltage-divider, or both).




Capacitors

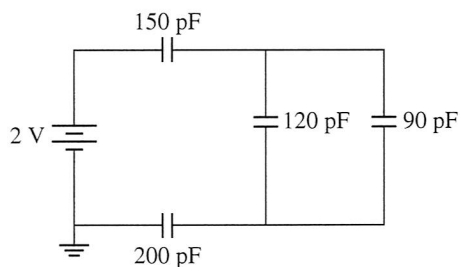
- 1-24. Find the equivalent capacitance at the input nodes and calculate the charge-discharge energy W for the parallel capacitors.



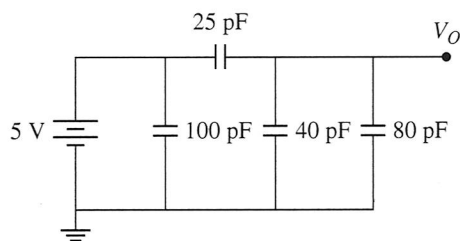
- 1-25. (a) What is the energy W needed to charge the circuit?
 (b) Write the capacitance voltage divider expression for V_O and solve for the value.



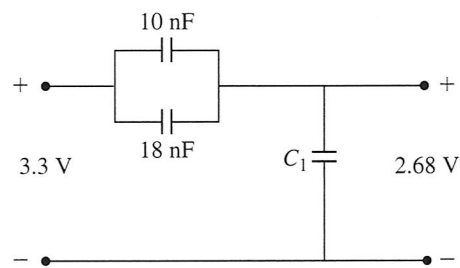- 1-26. Find C_1 and the energy to charge C_1 .




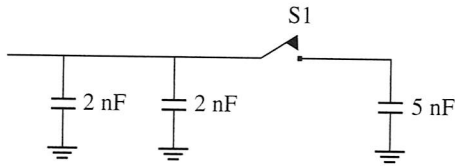- 1-27. The 2 nF capacitors are precharged to 3 V, and the 5 nF capacitor is precharged to 1.2 V. At $t = 0$, switch S1 closes. What is the final voltage?




Diodes

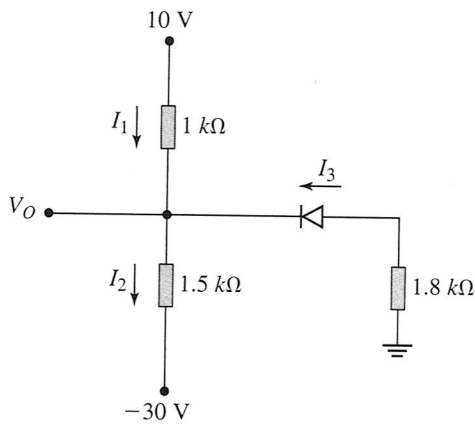
- 1-28. Calculate V_O and the current through each resistor. Assume that the forward bias diode voltage is 0.7 V.



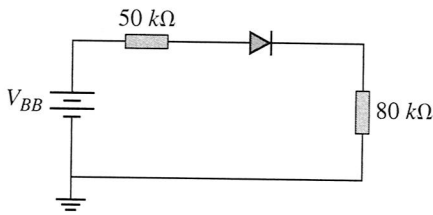
- 1-29. Given that $I_S = 10$ nA. Calculate I_D and V_D for (a) $V_{BB} = 1$ V and (b) $V_{BB} = 10$ V.



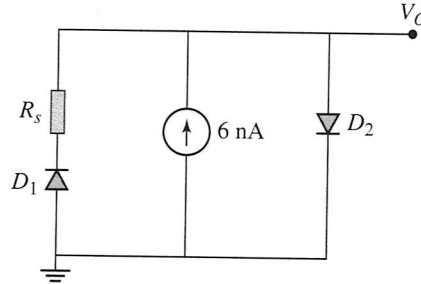
- 1-30. Calculate V_O given that the reverse bias saturation current $I_S = 1$ nA and you are at room temperature.



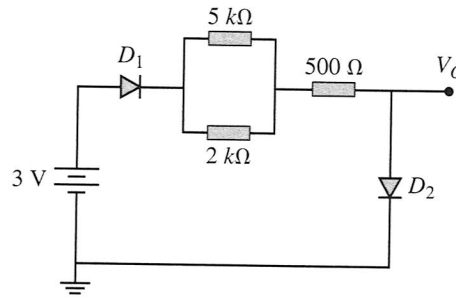- 1-31. Diode D_1 has a reverse bias saturation current of $I_{S1} = 1$ nA, and diode D_2 has $I_{S2} = 4$ nA. At room temperature, what is V_O ?



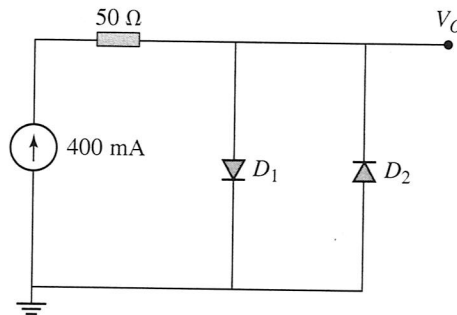- 1-32. Calculate the voltage across the diodes given that the reverse bias saturation current in D_1 is $I_{S1} = 175$ nA, and $I_{S2} = 100$ nA.



- 1-33. Given I_{D1}



- 1-34. Cal

+10 V