

SOLUTION

HoW. #02


1.21.

$$\begin{aligned} R_{eq} &= 2K + \left((3K \parallel 4K) + 5K \right) \parallel 7K \parallel 6K \\ &= 2K + (6.71K \parallel 3.23K) \\ &= 2K + 2.18K \\ &= 4.18K \end{aligned}$$

$$\therefore V_{2K} = \frac{2K \times 10V}{4.18K} = \boxed{4.78V}$$

1.22.

Step 1:-

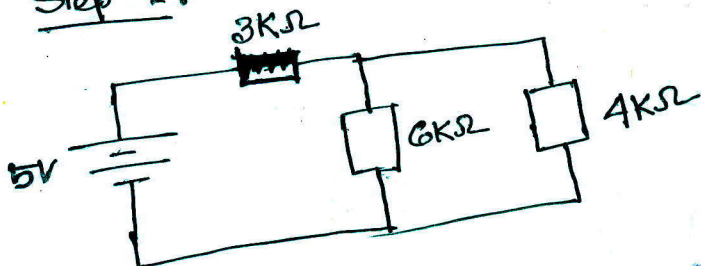


$$\begin{aligned} R_{eq} &= 3K + (6K \parallel 4K) \\ &= 5.4K \end{aligned}$$

$$I' = \frac{5V}{5.4K} = 0.925mA$$

$$\begin{aligned} \therefore I'_{6K} &= \frac{4K}{6K+4K} \times 0.925mA \\ &= 0.37mA \end{aligned}$$

Step 2:-

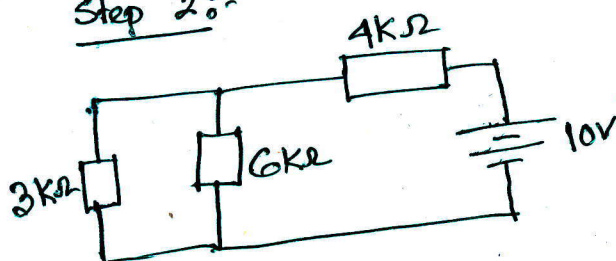

$$\begin{aligned} R_{eq} &= 4K + (6K \parallel 3K) \\ &= 6K \end{aligned}$$





$$I'' = \frac{10V}{6K} = 1.67mA$$

$$\begin{aligned} \therefore I''_{6K} &= \frac{3K}{6K+3K} \times 1.67mA \\ &= 0.55mA \end{aligned}$$

$$\therefore I_{6K} = I'_{6K} + I''_{6K} = 0.37mA + 0.55mA = \boxed{0.925mA}$$

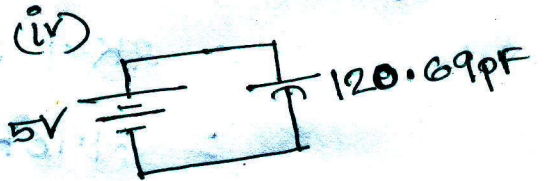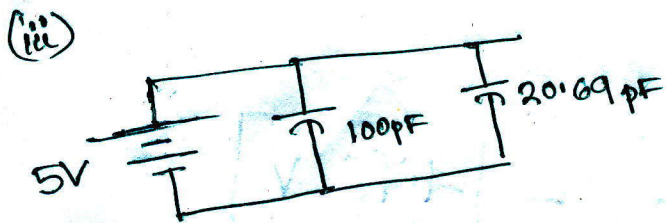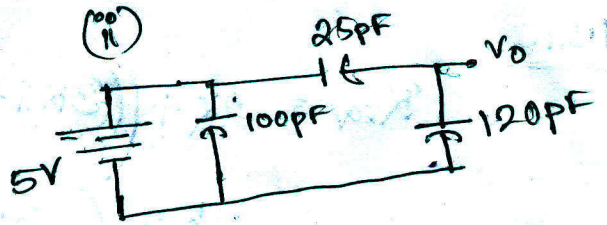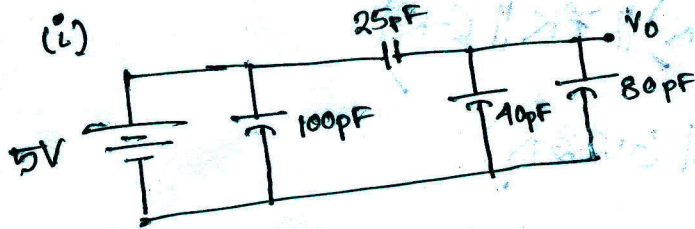1.25

$$C_{eq} = 100 \text{ pF} \parallel (25 \text{ pF} + (10 \text{ pF} \parallel 80 \text{ pF}))$$
$$= 100 \text{ pF} \parallel 25 \text{ pF}$$




(a)

$$W = \frac{1}{2} \times 120.69 \times 10^{-12} \times (5)^2$$
$$= \boxed{1.51 \text{ nJ}}$$

(b)

$$V_0 = \frac{25 \text{ pF}}{(120 + 25) \text{ pF}} \times 5 \text{ V}$$
$$= \boxed{0.862 \text{ V}}$$

1.26.

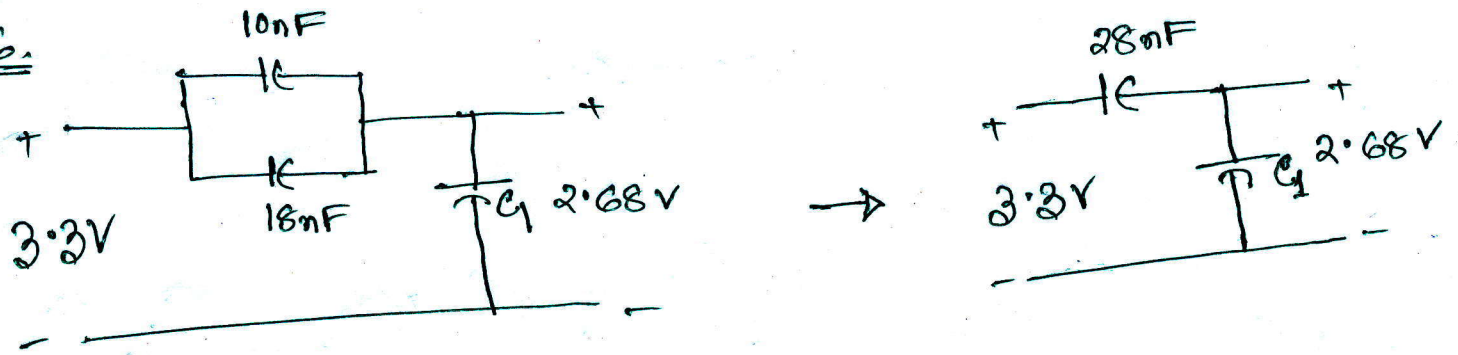

Now,

$$2.68 = \frac{28}{28 + C_1} \times 3.3 \text{ V}$$

$$\Rightarrow \frac{28}{28 + C_1} = \frac{2.68}{3.3}$$

$$\Rightarrow \frac{28 + C_1}{28} = \frac{3.3}{2.68}$$

$$\Rightarrow 28 + C_1 = 1.23 \times 28$$

$$\Rightarrow \boxed{C_1 = 6.48 \text{ nF}}$$

Now,

$$W = \frac{1}{2} \times 6.48 \times 10^{-9} \times (2.68)^2 = \boxed{23.27 \text{ nJ}}$$

1.27.

Here,

$$Q_{T \text{ before switching}} = Q_{T \text{ After switching}}$$

$$\Rightarrow C_1 V_1 + C_2 V_2 = (C_1 + C_2) V$$

$$\Rightarrow (2+2) \times 10^{-9} \times 3 + 5 \times 10^{-9} \times 1.2 = (2+2+5) \times 10^{-9} \times V$$

$$\Rightarrow \frac{(12+6) \times 10^{-9}}{9 \times 10^{-9}} = V$$

$$\Rightarrow V = \boxed{2 \text{ V}}$$

1.28.

$$I_1 + I_3 = I_2$$

$$\Rightarrow \frac{10 - V_0}{1K} + \frac{0 - (V_0 + 0.7)}{1.8K} = \frac{V_0 + 30}{1.5K}$$

$$\Rightarrow \frac{10 - V_0}{1} = \frac{V_0 + 0.7}{1.8} + \frac{V_0 + 30}{1.5}$$

$$\Rightarrow 27 - 2.7V_0 = 1.8V_0 + 54 + 1.5V_0 + 1.05$$

$$\Rightarrow 6V_0 = 27 - 54 - 1.05$$

$$= -28.05$$

$$\therefore \boxed{V_0 = -4.675 \text{ V}}$$

$$I_1 = \frac{10 + 4.675}{1K} = \boxed{14.675 \text{ mA}}$$

$$I_2 = \frac{-4.675 + 30}{1.5K} = \boxed{16.88 \text{ mA}}$$

$$I_3 = \frac{4.675 - 0.7}{1.8K} = \boxed{2.21 \text{ mA}}$$

1.29. (a) $V_{BB} = 1V$

KVL:-

$$-1 + 50K \times I_D + V_D + 80K \times I_D = 0$$

$$\Rightarrow V_D = 1 - 130K \times I_D$$

Now,

$$I_D = I_S \left(e^{\frac{V_D}{V_{th}}} - 1 \right)$$

$$= 10 \times 10^{-9} \left(e^{\frac{1 - 130K \times I_D}{0.026}} - 1 \right)$$

$$= f(I_D)$$

Solving Analytically,

$$\boxed{I_D = 6.4 \mu A}$$

$$\therefore \boxed{V_D = 0.168 \text{ V}}$$

I_D	$f(I_D)$
5 μA	7.01 mA
6 μA	47.28 μA
6.4 μA	6.4 μA

(b) $V_{BB} = 10 \text{ V}$

KVL:-

$$V_D = 10 - 130 \text{ K} \times I_D$$

Now.

$$I_D = 10 \times 10^{-9} \left(e^{\frac{10 - 130 \text{ K} \times I_D}{0.026}} - 1 \right)$$

$$= f(I_D)$$

Solving Analytically

$$\therefore I_D = 75.138 \mu\text{A}$$

$$\therefore V_D = 0.232 \text{ V}$$

I_D	$f(I_D)$
75 μA	$1.5 \times 10^{-4} \text{ A}$
75.1 μA	78.2 μA
75.138 μA	75.13 μA

I_D	$f(I_D)$
75 μA	35.4 μA