

$$V_{DS} = 0.8V$$

$$V_{GS} = 3V$$

$$V_{DS} < V_{GS} - V_t$$

$$0.8 < 3 - 0.5$$

$$0.8 < 2.5 \text{ [Linear region]}$$

a

$$K_n = 200 \mu A/V^2 ; W/L = 4 ; V_{th} = 0.5V ; V_D = 0.8V$$

$$I_D = K_n (W/L) [2 (V_{GS} - V_{th}) V_{DS} - V_{DS}^2]$$

$$= 200(4) \left[\frac{2(3-0.5)(0.8) - (0.8)^2}{2} \right] = \frac{2.68 \mu A}{2}$$


$$= 1.344 \mu A$$

b


Value of R_D

$$R_D = \frac{1.5 - V_D}{I_D} = \frac{1.5 - 0.8}{1.344}$$

$$= 266.45 \approx 520.83 \Omega$$

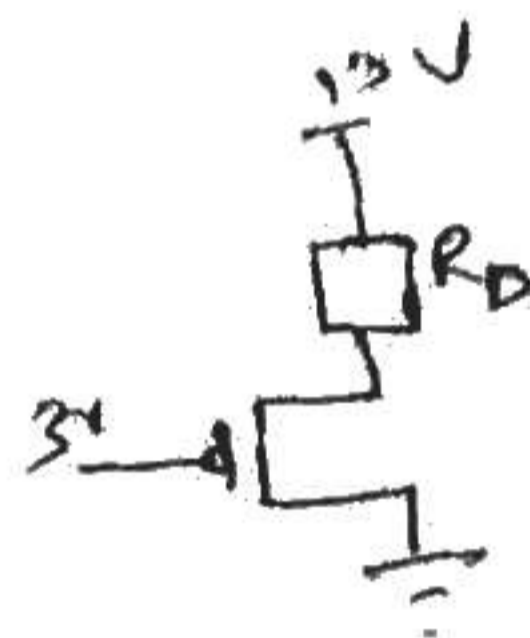

3.5

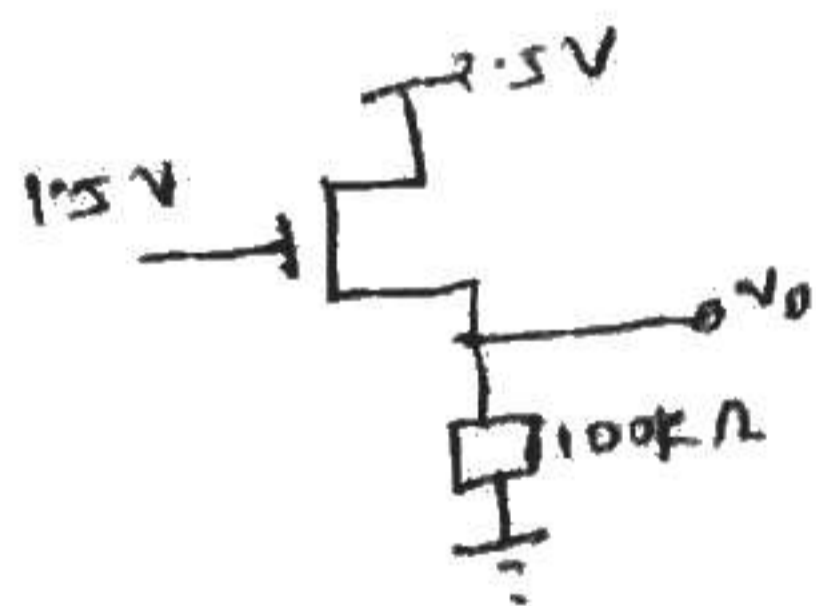

$$W/L = 3$$

$$V_{th} = 0.6V$$

$$K_n = 75 \mu A/V^2$$

find V_0 & I_D

$$V_{GS} = V_G - V_0$$

$$I_D = \frac{V_0}{100k}$$

$$I_D = \frac{K_n}{2} (W/L) (V_{GS} - V_t)^2$$

$$\frac{V_0}{100} = \frac{75}{2} (3) [(1.5 - V_0) - 0.6]^2$$

$$\boxed{V_0 = 0.658V}$$

$$I_D = \frac{V_0}{100k}$$

$$= \frac{0.658}{100k}$$

$$= 0.658 \mu A \times 10^{-5}$$

$$= 6.58 \times 10^{-6}$$

$$\boxed{I_D = 6.58 \mu A}$$

$$V_{DS} = 0.8 \text{ V}$$

$$V_{GS} = 3 \text{ V}$$

$$V_{DS} < V_{GS} - V_t$$

$$0.8 < 3 - 0.5$$

$$0.8 < 2.5 \text{ [Linear region]}$$

$$K_n = 200 \mu\text{A/V}^2; \quad W/L = 4; \quad V_{th} = 0.5 \text{ V}; \quad V_D = 0.8 \text{ V}$$

$$I_D = K_n (W/L) \left[2 (V_{GS} - V_{th}) V_{DS} - V_{DS}^2 \right]$$

$$= 200(4) \left[\frac{2(3-0.5)(0.8) - (0.8)^2}{2} \right] = \frac{2.68 \mu\text{A}}{2}$$


$$= 1.34 \mu\text{A}$$

(b)


Value of R_D

$$R_D = \frac{1.5 - V_D}{I_D} = \frac{1.5 - 0.8}{1.344}$$

$$= 520.83 \Omega$$

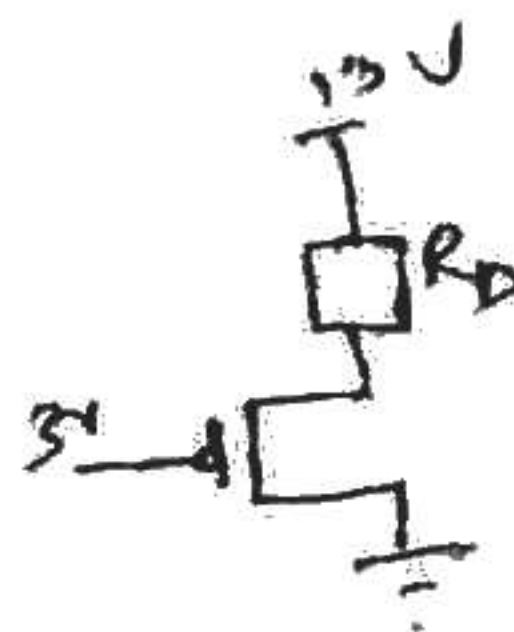

3.5

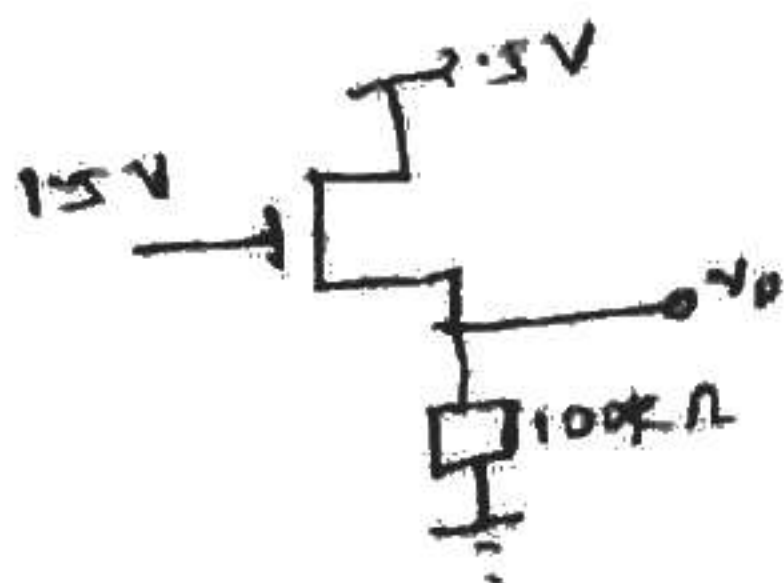

$$W/L = 3$$

$$V_{th} = 0.6 \text{ V}$$

$$K_n = 75 \mu\text{A/V}^2$$

find V_o & I_D

$$V_{GS} = V_G - V_S$$

$$I_D = \frac{V_o}{100k}$$

$$I_D = \frac{K_n}{2} (W/L) (V_{GS} - V_t)^2$$

$$\frac{V_o}{100k} = \frac{75}{2} (3) \left[(1.5 - V_o) - 0.6 \right]^2$$

$$\boxed{V_o = 0.658 \text{ V}}$$

$$I_D = \frac{V_o}{100k}$$


$$= \frac{0.658}{100k}$$

$$= 0.658 \mu\text{A} \times 10^6$$

$$= 6.58 \times 10^5$$

$$\boxed{I_D = 6.58 \mu\text{A}}$$

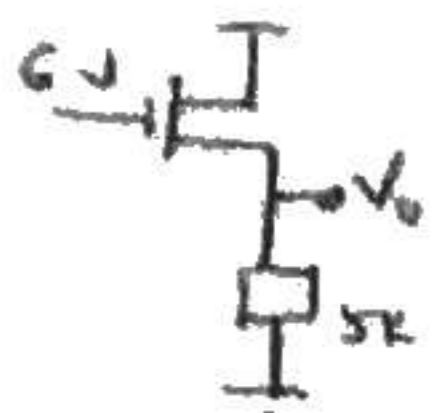3.6 $V_{th} = 0.8V$
 $K_n = 200 \mu A/V^2$
 $W/L = 4$
 $V_0 = ?$



$$I_D = \frac{V_0}{5k}$$

$$V_{GS} = V_G - V_S = 6 - V_0$$

$$V_{DS} = V_D - V_S = 5 - V_0$$

$$V_{GS} - V_{th} > V_{DS}$$

$$6 - V_0 - 0.8 > 5 - V_0$$

$5.2 > 5$ [Linear region]

$$I_D = K_n' (W/L) \left[\frac{2(V_{GS} - V_{th})V_{DS} - (V_{DS})^2}{2} \right]$$

$$\frac{V_0}{5} = 200(4) \left[\frac{2(6 - V_0 - 0.8)(5 - V_0) - (5 - V_0)^2}{2} \right]$$

$$V_0 = 3.806V$$

3.10

$$K_n' = 250 \mu A/V^2$$


$$V_{th} = 0.5V$$

$$W/L = 3$$

$$I_{DS} = \frac{K_n'}{2} (W/L) (V_{GS} - V_{th})^2$$

$$= \frac{250 \times 10^{-6}}{2} (3) (2 - 0.5)^2$$

$$I_D = 0.84375 mA$$

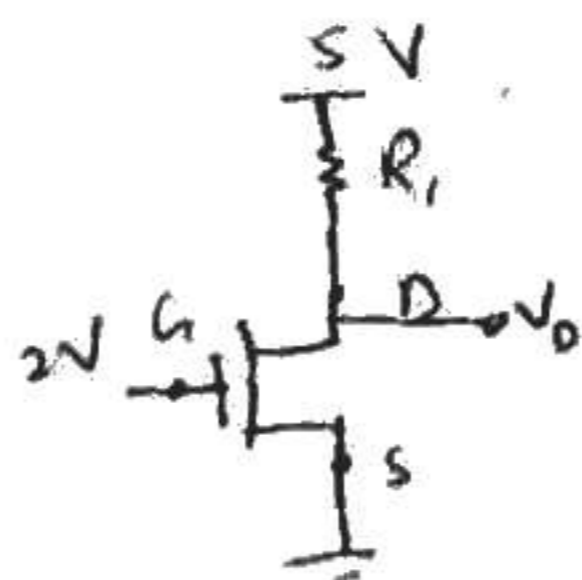

$$V_{DS} = V_{DS} - V_{th}$$

$$V_0 - V_S = V_G - V_S - V_{th}$$

$$V_0 = V_G - V_{th}$$

$$V_0 = 2 - 0.5 = 1.5V$$

$$R_D = \frac{V_{DD} - V_0}{I_{DS}} = \frac{5 - 1.5}{0.84375 \times 10^{-3}}$$

$$R_D = 4.148 k\Omega$$


3.11

$$K_n = 250 \mu A/V^2$$

$$V_{th} = 0.5V$$

$$W/L = 3$$

$$V_G = 0$$

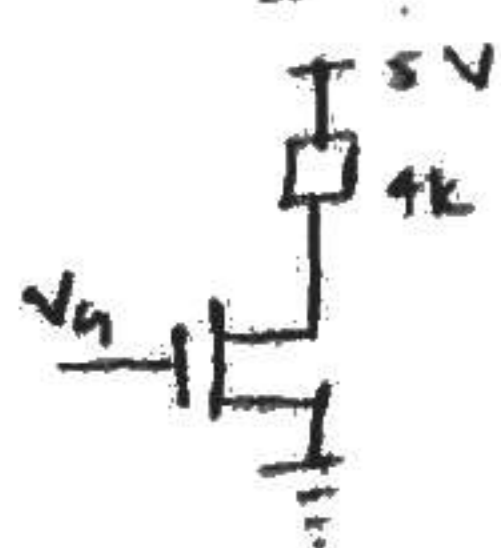

$$V_0 = V_G - V_{th}$$

$$V_0 = V_G - 0.5$$

$$I_D = \frac{5 - V_0}{4k} = \frac{5.5 - V_G}{4k}$$

$$\frac{5.5 - V_0}{4k} = (250 \times 10^{-6}) (3) (V_G - 0.5)^2$$

$$5.5 - V_G = 3V_G^2 - 3V_G + 0.75$$

$$V_G = 3V_G^2 - 3V_G - 4.75$$


$$3V_G^2 - 4V_G - 4.75 = 0$$

$$V_G = 2.09V$$

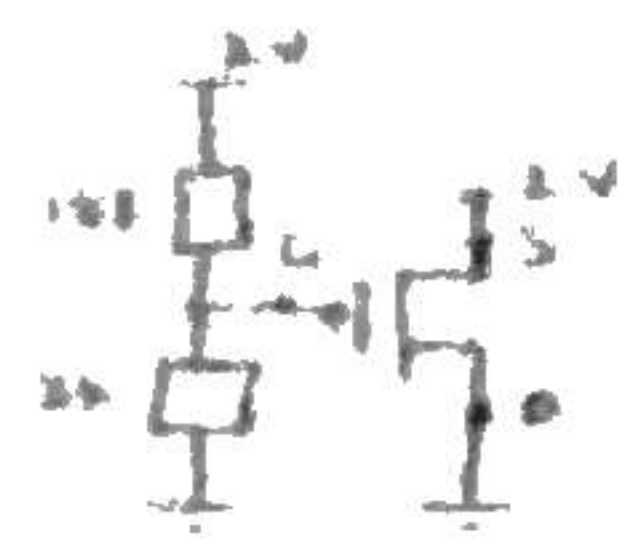
3.15



$V_{gs} = 0.4V$
 $\mu/L = 4$
 $k_p' = 100 \mu A/V^2$
 $V_{ds} = 10 \left(\frac{2k}{2+8} \right) = 2V$
 $V_{ds} = V_d - V_s = 2 - 2 = 0$
 $V_{ds} > V_{gs}$
 So $I_{ds} = 0$




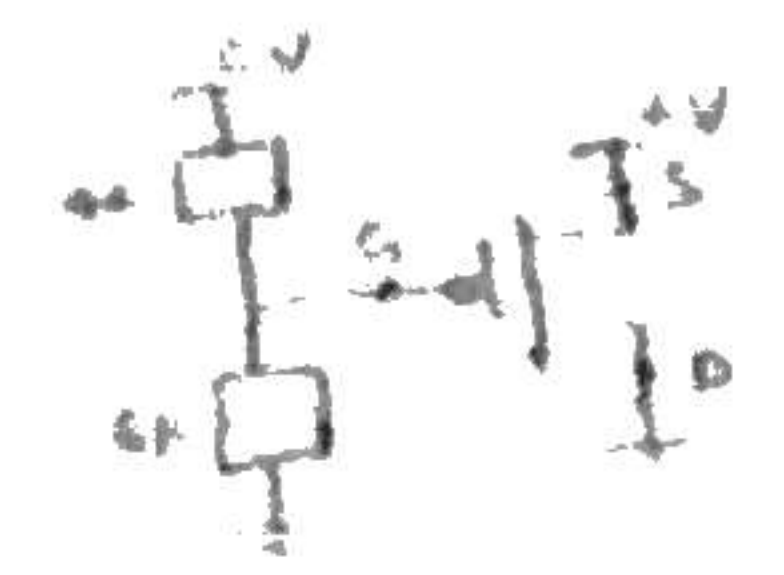$V_{gs} = 2 \left(\frac{2}{2+8} \right) = 0.2V$
 $V_{ds} < V_{gs} - V_{tp}$
 $-2 < -1.8 + 0.4$
 $-2 < -1.4$
 saturation mode
 $I_D = \frac{k_p'}{2} (\mu/L) (V_{gs} - V_{tn})^2$
 $= \frac{100}{2} (4) (-1.4)^2$
 $= 200 (1.96)$
 $I_D = 392 \mu A$



$V_{gs} = 2 \left(\frac{6}{10} \right) = 1.2V$
 $V_{ds} < V_{gs} - V_{tp}$
 $-2 < (1.2 - 2) + 0.4$
 $-2 < (-0.8 + 0.4)$
 $-2 < -0.4$
 Saturation mode
 $I_D = \frac{k_p'}{2} (\mu/L) (V_{gs} - V_{tn})^2$
 $= \frac{100}{2} (4) (0.16)$
 $I_D = 32 \mu A$

3.21

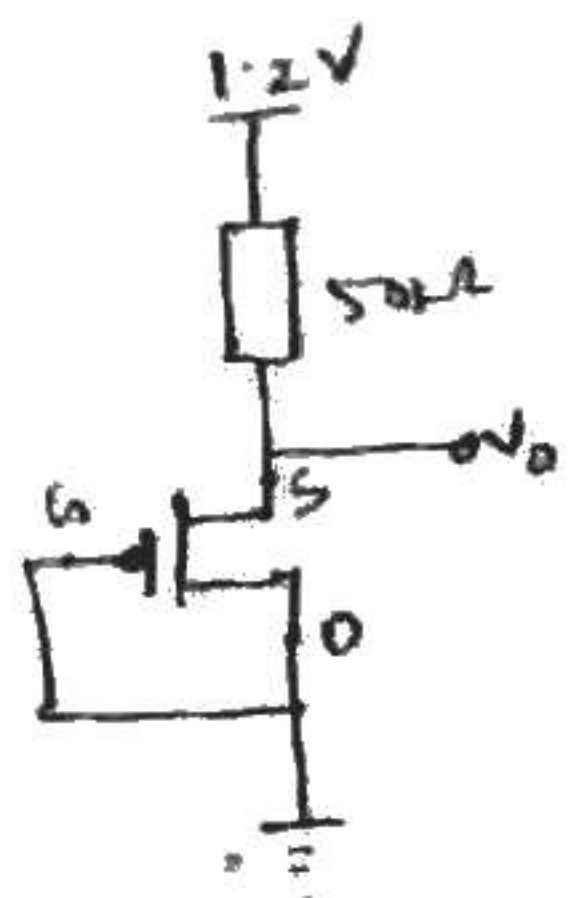


$\mu/L = 6$
 $V_{tp} = -0.3V$
 $k_p = 40 \mu A/V^2$
 $V_0, I_D \Rightarrow ?$

$|V_{gs} - V_{ts}| < |V_{ds}|$
 $V_0 - V_t < V_0 \rightarrow \text{saturation}$

$I_D = \frac{k_p'}{2} (\mu/L) [V_{gs} - V_{ts}]^2$
 $\frac{V_0 - 1.2}{50k} = \frac{40}{2} (6) (V_0 + 0.3)^2$

$\frac{V_0 - 1.2}{50k} = 120 (V_0^2 + 0.07 + 0.6V_0) \times 10^{-6}$
 $V_0 - 1.2 = 50 \times 120 \times 10^{-3} (V_0^2 + 0.09 + 0.6V_0)$
 $V_0 - 1.2 = 6000 \times 10^{-3} (V_0^2 + 0.09 + 0.6V_0)$
 $V_0 - 1.2 = 6V_0^2 + 3.6V_0 + 0.54$
 $6V_0^2 + 2.64V_0 + 1.74 = 0$
 $V_0 \rightarrow 0.1066V_0 + 0.29 = 0$
 $V_0 = 0.27V, -0.1096V$

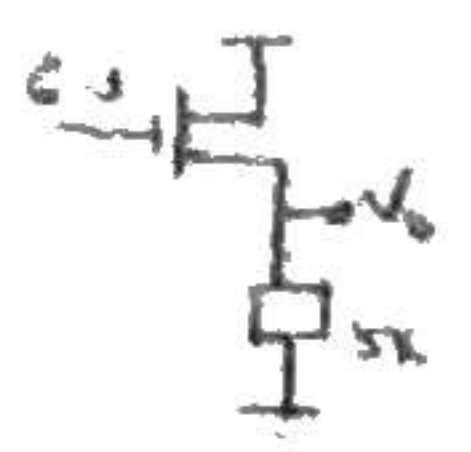3.6 $V_{th} = 0.8V$
 $K_n = 200 \mu A/V^2$
 $W/L = 4$
 $V_0 = 0$



$I_D = \frac{V_0}{5k}$
 $V_{GS} = V_G - V_S = 6 - V_0$
 $V_{DS} = V_D - V_S = 5 - V_0$
 $V_{GS} - V_{th} > V_{DS}$
 $6 - V_0 - 0.8 > 5 - V_0$
 $5.2 > 5$ [Linear region]


$$I_D = K_n' (W/L) \left[\frac{2(V_{GS} - V_{th})V_{DS} - (V_{DS})^2}{2} \right]$$

$$\frac{V_0}{5} = 200(4) \left[\frac{2(6 - V_0 - 0.8)(5 - V_0) - (5 - V_0)^2}{2} \right]$$

$V_0 = 3.806V$

3.10 $K_n' = 250 \mu A/V^2$
 $V_{th} = 0.5V$
 $W/L = 3$
 $I_{D0} = \frac{K_n'}{2} (W/L)_n (V_{GS} - V_{th})^2$
 $= \frac{250 \times 10^{-6}}{2} (3) (2 - 0.5)^2$

$I_D = 0.84375mA$

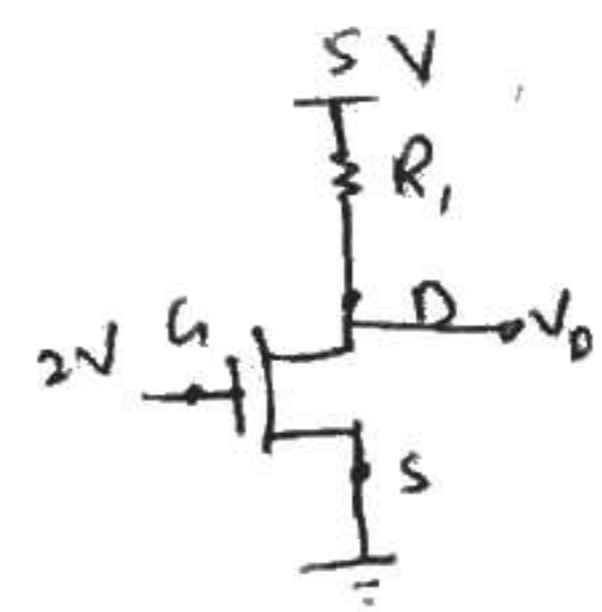

$V_{DS} = V_{GS} - V_{th}$
 $V_D - V_S = V_G - V_S - V_{th}$
 $V_0 = V_G - V_{th}$
 $V_0 = 2 - 0.5 = 1.5V$
 $R_D = \frac{V_{DD} - V_D}{I_{D0}} = \frac{5 - 1.5}{0.84375 \times 10^{-3}}$

$R_D = 4.448k\Omega$

3.11 $K_n = 250 \mu A/V^2$
 $V_{th} = 0.5V$
 $W/L = 3$
 $V_G = 0$

$V_D = V_G - V_{th}$
 $V_0 = V_G - 0.5$

$I_D = \frac{5 - V_D}{4k} = \frac{5 - 5 - V_{th}}{4k}$

$$\frac{5.5 - V_G}{4k} = (250 \times 10^{-6}) (3) (V_G - 0.5)^2$$

$$5.5 - V_G = 3V_G^2 - 3V_G + 0.75$$

$$V_G = 3V_G^2 - 3V_G - 4.75$$


$$3V_G^2 - 4V_G - 4.75 = 0$$

$V_G = 2.09V$

$$\bar{I}_D = \frac{(1.2 - 0.27)V}{50k}$$

$$\bar{I}_D = 0.0186mA$$

$$\bar{I}_D = 18.6\mu A$$

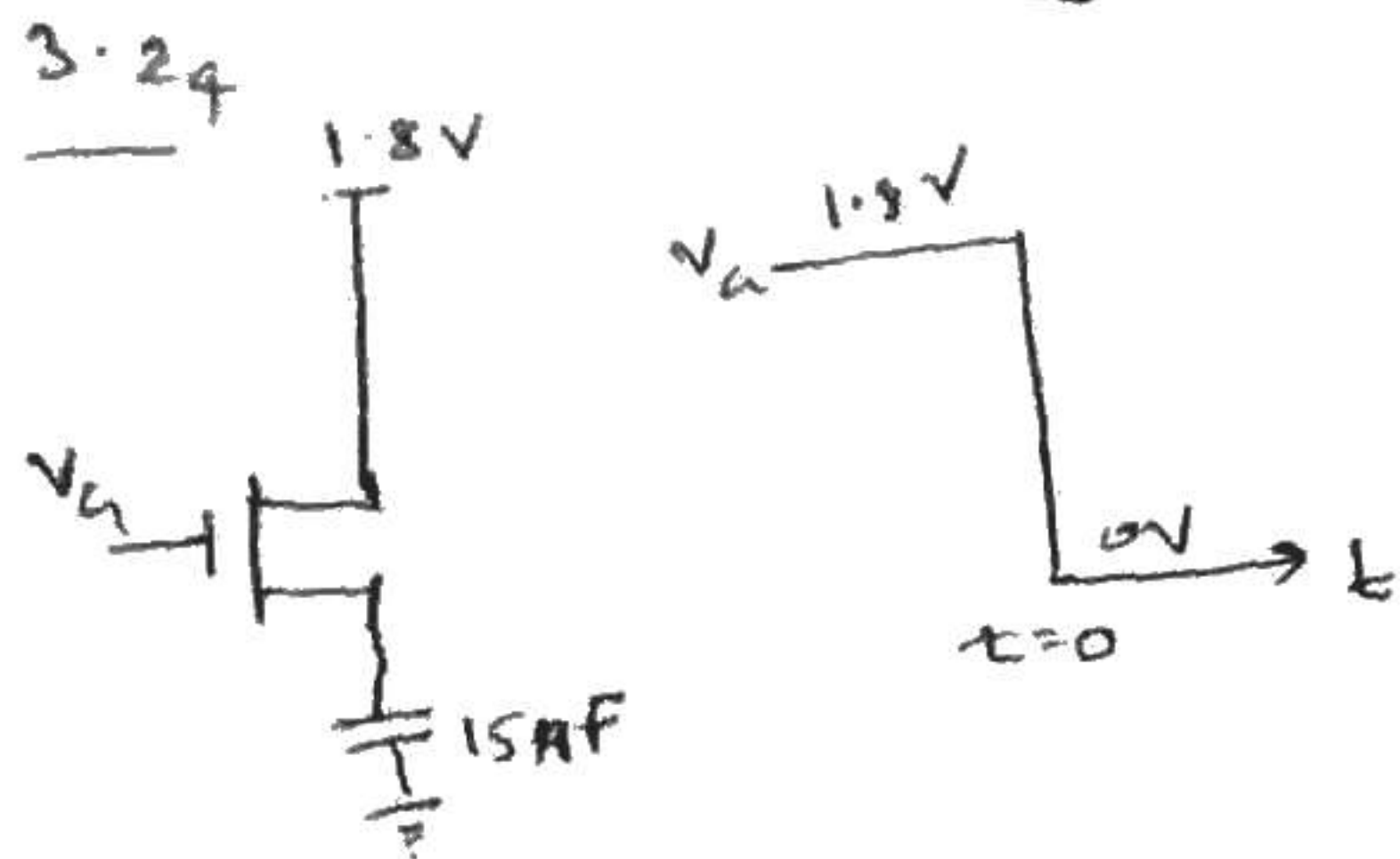

(a) $K_p = 40 \mu A/V^2$

$$V_{tp} = -0.4V$$

$$W/L = 5$$

$$V_{GS} = V_G - V_S = 0 - 1.8$$

$$= -1.8V @ t=0^+$$

$$|I_{DS}| = \frac{K_p}{2} (W/L)_p (|V_{GS}| - |V_{TP}|)^2$$

$$= \frac{40 \times 10^{-6}}{2} (5) (1.8 - 0.4)^2$$

$$\bar{I}_{DS} = 196\mu A$$

(b) No current flows through the capacitor

∴ non-saturation @ Linear region

(c) $W = \frac{1}{2} C V^2 = \frac{1}{2} (15 \times 10^{-9}) (1.8)^2$

$$W = 24.3nJ$$