

3.25. From given conditions,

$$V_{tp} = -0.4, K_p = 50 \mu\text{A/V}^2, \frac{W}{L} = 8, P_R = 10 \mu\text{W}$$

$$P_R = \frac{\Delta V^2}{R} = \frac{(2.2 - V_S)^2}{R} = 10 \mu\text{W}$$

$$\therefore R = \frac{(2.2 - V_S)^2}{10 \mu\text{W}} \quad \text{--- (1)}$$

Transistor is biased at the boundary,

$$\therefore V_{DS} = V_{GS} - V_{tp} \Rightarrow V_{\Delta} - V_S = V_G - V_S - V_{tp}$$

$$V_G = V_{tp} + V_{\Delta} = 0.5 - 0.4 = 0.1 \text{ V}$$

$$\begin{aligned} \text{also, } |I_D| &= \frac{K_p'}{2} \left(\frac{W}{L}\right) (V_{GS} - V_{tp})^2 = \frac{K_p'}{2} \left(\frac{W}{L}\right) (V_G - V_S - V_{tp})^2 \\ &= \frac{50 \mu\text{A/V}^2}{2} (8) (0.1 - V_S - (-0.4))^2 = \frac{50 \mu\text{A/V}^2}{2} (8) (0.5 - V_S)^2 \quad \text{--- (2)} \end{aligned}$$

$$\text{Also } |I_D| = \frac{2.2 - V_S}{R} \quad \xrightarrow{\text{Combine (1)}} \quad \frac{2.2 - V_S}{\frac{(2.2 - V_S)^2}{10 \mu\text{W}}} = \frac{10 \mu\text{W}}{2.2 - V_S} \quad \text{--- (3)}$$

$$\therefore (2) = (3), \quad |I_D| = |I_D|$$

$$\therefore \frac{50 \mu\text{A/V}^2}{2} (8) (0.5 - V_S)^2 = \frac{10 \mu\text{W}}{2.2 - V_S}$$

$$\text{Get } V_S = 0.6815 \text{ V}, \quad \therefore V_S > V_D, \quad \therefore V_S \neq 0.336 \text{ V}$$

$$\text{From (1), } R = \frac{(2.2 - V_S)^2}{10 \mu\text{W}} = \frac{(2.2 - 0.6815)^2}{10 \mu\text{W}} = \underline{\underline{230.6 \text{ k}\Omega}}$$

3.26

$$(a) \quad V_{GS} = V_G - V_S = 0 - V_S$$

Assume saturation,

$$|I_{DS}| = \frac{7.5 \text{ mA}}{2} (5) (-V_S + 0.6)^2 = \frac{3 - V_S}{4 \text{ k}\Omega} = I_{DS}$$

$$\therefore \frac{3 - V_S}{4 \text{ k}\Omega} = (187.5 \cdot 10^{-4}) (V_S^2 - 1.2V_S + 0.36)$$

$$\therefore \underline{V_S = 1.842 \text{ V}} \quad \because \text{for PMOS } V_S > 0 \text{ V}_G$$

$$(b) \quad I_{DS} = \frac{3 - V_S}{4 \text{ k}\Omega} = \frac{3 - 1.842}{4 \text{ k}\Omega} = 289.5 \cdot 10^{-4} \text{ A}$$

$$I_{DS} = \frac{V_D}{2 \text{ k}\Omega} \Rightarrow V_D = (2 \text{ k}\Omega) (289.5 \cdot 10^{-4}) = 0.579 \text{ V}$$

$$|V_{DS}| > |V_{GS}| - |V_{Tp}|$$

$1.263 > 1.242$, so saturation is true.

$$\text{Thus, } \underline{\underline{V_D = 0.579 \text{ V}}}$$

3.30

$$V_{GS} = V_G - V_S = 0 - (-1) = 1 \text{ V}$$

Since $V_{DS} > V_{GS} - V_{Tn}$, i.e. $(2 > 1 - 0.6)$

\therefore NMOS is in Saturation,

$$\begin{aligned} \therefore I_{DS} &= \frac{K_n}{2} \left(\frac{W}{L}\right) (V_{GS} - V_{Tn})^2 = \frac{200 \cdot 10^{-6}}{2} (3) (1 - 0.6)^2 \\ &= 48 \text{ mA} \end{aligned}$$

$$R_1 = \frac{V_{DD} - V_D}{I_{DS}} = \frac{3 - 1}{48 \text{ mA}} = \underline{\underline{41.67 \text{ k}\Omega}} = R_2$$

3.35

$$V_G = V_D = V_O \Rightarrow V_{DS} = V_{GS}$$

Transistor is saturated because drain & gate are connected.

$$I_{DS} = \frac{K_n'}{2} \left(\frac{W}{L}\right) (V_{GS} - V_{Tn})^2 = \frac{90 \text{ mA}}{2} (10) (V_{DS} - 0.5)^2$$

$$I_{DS} = \frac{2.5 - V_D}{5 \text{ k}} = \frac{V_S}{2 \text{ k}} = I_{DS} \Rightarrow V_D - V_S = V_{DS} = 2.5 - 5I_{DS} - 2I_{DS}$$

$$\therefore I_{DS} = \frac{90 \text{ mA}}{2} (10) (2.5 - 5I_{DS} - 2I_{DS} - 0.5)^2 = 0$$

Then get, $I_D = 192.32 \text{ mA}$, or $I_D = 424.46 \text{ mA}$

Since it is saturation, $\underline{\underline{I_D = 192.32 \text{ mA}}}$


$$\text{For } V_O, I_D = \frac{2.5 \text{ V} - V_O}{5 \text{ k}\Omega} \Rightarrow V_O = 2.5 \text{ V} - I_D (5 \text{ k}\Omega)$$

$$V_O = 2.5 - (192.32 \text{ mA})(5 \text{ k}\Omega) = \underline{\underline{1.54 \text{ V}}}$$

$$3.37 \quad V_T = V_{T0} + \gamma \left(\sqrt{|2\phi_F + V_{SB}|} - \sqrt{|2\phi_F|} \right)$$

$$\sqrt{|2\phi_F + V_{SB}|} = \sqrt{|2\phi_F|} + \frac{V_T - V_{T0}}{\gamma} \rightarrow V_{SB} = \left(\sqrt{|2\phi_F|} + \frac{V_T - V_{T0}}{\gamma} \right)^2 - |2\phi_F|$$
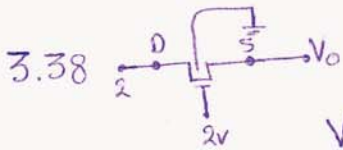
$$V_{SB} = 86.17 \text{ mV} \rightarrow V_{BS} = -86.17 \text{ mV}$$



$$V_T = V_{T0} + \gamma \left(\sqrt{2\phi_F + V_{SB}} - \sqrt{2\phi_F} \right)$$

$$\left. \begin{aligned} V_T &= 0.6 \text{ V} + 0.25 \left(\sqrt{0.7 + V_o} - \sqrt{0.7} \right) \\ (\text{Maximum } V_o) &= V_{dd} - V_T \rightarrow V_T = 2 - V_o \end{aligned} \right\} \Rightarrow \begin{aligned} V_o &= 1.26 \text{ V} \\ V_T &= 0.74 \text{ V} \end{aligned}$$