


References

[1] F. A. Linholm IEEE J. Solid State Circuits, SC-10, 2, pp. 106–109, April 1975.

Exercises


Inverter Static Voltage Characteristics

 5-1. A CMOS inverter has $V_{DD} = 1.2$ V. $V_{OH} = 1.15$ V, $V_{OL} = 0.15$ V, $V_{IH} = 1.05$ V, and $V_{IL} = 0.2$ V. Calculate NM_H , NM_L and draw the noise margin map with appropriate labels of numbers.




5-2. A logic gate noise margin parameters are: $V_{IH} = 1.6$ V, $V_{IL} = 0.3$ V, $V_{OH} = 1.7$ V, and $V_{OL} = 0.2$ V.
 (a) Calculate NM_H .
 (b) Calculate NM_L .
 (c) The input voltage is down to 1.7 V and a negative 50 mV noise spike appears. What happens to the circuit fidelity?
 (d) The input voltage is down to 1.7 V and a negative 150 mV noise spike appears. What happens to the circuit fidelity?

 
5-3. Given the logic gate noise margins: $NM_H = 100$ mV, $NM_L = 75$ mV, and $V_{DD} = 2$ V.
 (a) If $V_{IH} = 1.75$ V, what is V_{OH} ?
 (b) If $V_{IL} = 0.3$ V, what is V_{OL} ?



 5-4. A CMOS inverter uses $V_{DD} = 0.9$ V. $V_{OH} = 0.8$ V, and $V_{OL} = 0.1$ V. If the noise margins must be 20% of V_{DD} , what are V_{IL} and V_{IH} ? Draw the noise margin map and label.





 5-5. Graphically determine the change in logic threshold of the CMOS inverter transfer curve in the figure if the curve shifts 0.2 V to the right in the midregion.



5-6. (a) Design the W_p/W_n ratios of a CMOS inverter for symmetrical static voltage transfer characteristic. $\mu_n = 1400$ $\text{cm}^2/\text{V} \cdot \text{s}$, $\mu_p = 500$ $\text{cm}^2/\text{V} \cdot \text{s}$, $V_m = 0.35$ V, $V_{tp} = -0.35$ V, and $V_{DD} = 1.3$ V.

(b) Redesign if $V_{tp} = -0.45$ V.

  

5-7. An inverter with a symmetrical voltage transfer curve has a restriction that $W_p/W_n = 4.6$. $V_{DD} = 1.2$ V, $\mu_n = 1530$ cm²/V · s, $\mu_p = 540$ cm²/V · s, and $V_{tp} = -0.4$. What must V_m be set to satisfy this condition?

5-8. A CMOS inverter has transistor parameters: $K_n(W/L)_n = 100$ $\mu\text{A}/\text{V}^2$, $K_p(W/L)_p = 300$ $\mu\text{A}/\text{V}^2$, $V_{tn} = 0.7$ V, $V_{tp} = -0.75$ V, and $V_{DD} = 2.5$ V. What fraction of the total output voltage swing will the nMOS transistor be in saturation?

5-9. A CMOS inverter has its nMOS transistor in nonsaturation and its pMOS transistor in saturation. Given $K_n = 50$ $\mu\text{A}/\text{V}^2$, $K_p = 25$ $\mu\text{A}/\text{V}^2$, $V_{tn} = 0.5$ V, $V_{tp} = -0.6$ V, $(W/L)_n = 2$, $(W/L)_p = 4$, $I_{DD} = 11$ μA , and $V_{DD} = 2$ V, calculate the inverter output voltage V_O .


Inverter Static Current Characteristics

5-10. Given an inverter with $V_{DD} = 1.5$ V, $V_m = 0.4$ V, and $V_{tp} = -0.4$ V, calculate the peak current during the transition if $(W/L)_n = 3$, $(W/L)_p = 7.5$, $K_p = 50$ $\mu\text{A}/\text{V}^2$, and $K_n = 125$ $\mu\text{A}/\text{V}^2$.

5-11. An inverter has $V_{DD} = 2$ V, $V_m = 0.5$ V, $V_{tp} = -0.5$ V, $K_n = 300$ $\mu\text{A}/\text{V}^2$, $K_p = 200$ $\mu\text{A}/\text{V}^2$, $(W/L)_n = 2$, and $(W/L)_p = 3$.

- (a) If $V_{IN} = 0.8$ V, what is I_{DD} ?
- (b) The I_{DD} solution in part (a) appears twice in the current transfer curve. Use the pMOS equations to calculate the other V_{IN} value to satisfy the current in part (a).

 5-12. Given $V_{DD} = 1.5$ V, $K_p = 70$ μA , $K_n = 120$ μA , $(W/L)_p = 150$, and $(W/L)_n = 75$, use the ITC to calculate V_{tp} .



5-13. Given that $V_{DD} = 1.8$ V, $V_m = 0.5$ V, and $K_n = 100$ $\mu\text{A}/\text{V}^2$, what is W/L of the nMOS transistor?

