

# ECE321 – Electronics I

## Lecture 10: Basic Digital Circuits with nMOSFET

---

**Payman Zarkesh-Ha**

*Office: ECE Bldg. 230B*

*Office hours: Tuesday 2:00-3:00PM or by appointment*

*E-mail: [payman@ece.unm.edu](mailto:payman@ece.unm.edu)*

## *Review of Last Lecture*

---



- Subthreshold Conduction (leakage)
- Velocity Saturation
- Threshold Voltage Roll-off
- Drain Induced Barrier Lower Effect (DIBL)
- Hot Electron

## Today's Lecture

- ❑ BASIC CMOS Inverter
  - Resistive load inverter
- ❑ Introduction to SPICE

  
## Resistive Load Inverter

- ❑ A resistive load inverter consists of a pull down NMOS and a pull up resistor
  - Voltage Transfer Characteristic (VTC) is a function of transistor size and resistor value
  - A good inverter provide a fast transition in VTC curve



 
## Resistive Load Inverter Design

- The pull up resistor must be calculated to maintain a specific low level voltage ( $V_{OL}$ ) at the output
- Example:
  - $K'_n = 100 \mu\text{A}/\text{V}^2$
  - $V_{T0} = 0.7 \text{ V}$
  - $V_{OL} = 0.25 \text{ V}$
- How to compute  $R_L$  as a function of  $(W/L)$ ?
- How much is  $R_L$  for  $(W/L)=5$  ?


 
## Power in Resistive Load Inverter

- When the output is high, there is no current drawn from  $V_{DD}$
- When the output is high, a DC current is drawn from  $V_{DD}$
- Assuming probability is 50% for logic high and logic low
- How to compute Power in the previous example?



- How much is the power for a design with 100K similar resistive load logic gate?

## Overview of TSPICE (input file)


\* Test Circuit for VLSI Class

Vdd Vp gnd DC 5V

RL Vp Vout 10K

M1 Vout Vin gnd gnd CMOSN W=8um L=1.6um

Vin Vin gnd DC 5V

 

.DC Vin 0 5 0.05

.plot Vout

.model CMOSN NMOS LEVEL=1 VTO=0.7 KP=100U GAMMA=0.1  
LAMBDA=0.01 PHI=0.3

.end

## Overview of TSPICE (output waveform)

