

# ECE321 – Electronics I

## Lecture 12: CMOS Inverter: Noise Margin & Delay Model

---

**Payman Zarkesh-Ha**

Office: ECE Bldg. 230B  
Office hours: Tuesday 2:00-3:00PM or by appointment  
E-mail: [payman@ece.unm.edu](mailto:payman@ece.unm.edu)

## *Review of Last Lecture*


---

- CMOS Inverter
- Voltage Transfer Characteristics (VTC)
  - Switching threshold voltage
  - Output high voltage
  - Output low voltage
  - Input high voltage
  - Input low voltage
- Current Transfer Characteristics (ITC)
  - Peak current

## Today's Lecture


- Noise Margin Definition
- Approximation of Noise Margin for CMOS Inverter
- Propagation Delay
- Rise and Fall Times
- Input and Self Loading (Load) Capacitances
- Delay Approximation
 
## Review: Voltage Transfer Characteristics



 
### Important Parameters on VTC:

- Switching Threshold Voltage  $V_S$  or  $V_M$
- Gain at  $V_S$  or  $V_M$
- Output High Voltage  $V_{OH}$
- Output Low Voltage  $V_{OL}$
- Input High Voltage  $V_{IH}$
- Input Low Voltage  $V_{IL}$



## Effect of Noise on a CMOS Inverter

 


ECE321 - Lecture 12

University of New Mexico

Slide: 5


## Noise Margin

 

### □ Noise Margin

$$NM_H = V_{OH} - V_{IH}$$

$$NM_L = V_{IL} - V_{OL}$$

 

### □ It is better to have:


- $V_{OH} = V_{DD}$
- $V_{OL} = V_{SS}$
- Large  $NM_H$
- Large  $NM_L$

ECE321 - Lecture 12


University of New Mexico

Slide: 6

## Noise Margin in Inverter and Buffer

 

VTC of an inverter

 

VTC of a buffer


## Example: Noise Margin Calculation

An IC with  $V_{DD} = 1.5$  V shows  $V_{OH} = 1.35$  V,  $V_{OL} = 0.2$  V,  $V_{IH} = 1.2$  V, and  $V_{IL} = 0.3$  V. Calculate the  $NM_L$  and  $NM_H$  for this IC.

Sketch the NM rectangles

$$NM_H = 1.35 - 1.2 = 150 \text{ mV}$$

$$NM_L = 0.3 - 0.2 = 100 \text{ mV}$$

 

## Noise Margin Approximation

- How to compute Noise Margin
  - Usually it is harder to compute the exact value of NM
  - Use approximation (gain factor)
  - Determine gain at  $V_M$
  - Extrapolate  $V_{IL}$  and  $V_{IH}$
  - $V_{OL}$  and  $V_{OH}$  are easy to compute

□ Example:

- $NM_L$  and  $NM_H$  in CMOS inverter


$$V_{IH} - V_{IL} = -\frac{(V_{OH} - V_{OL})}{g} = \frac{-V_{DD}}{g}$$

$$V_{IH} = V_M - \frac{V_M}{g} \quad V_{IL} = V_M + \frac{V_{DD} - V_M}{g}$$

$$NM_H = V_{DD} - V_{IH} \quad NM_L = V_{IL}$$

- where

$$g = \frac{-2}{\lambda_n + |\lambda_p|} \left( \frac{1}{V_M - V_{Tn}} + \frac{1}{V_{DD} - V_M - |V_{Tp}|} \right)$$

 

## Example: Noise Margin Approximation

- A CMOS inverter has  $V_{DD}=5V$  is designed to have  $V_M=2.9V$ . If  $V_{Tn}=0.7$ ,  $V_{Tp}=-0.5$ ,  $\lambda_n=0.05 V^{-1}$  and  $\lambda_p=-0.08 V^{-1}$ . Find the noise margins  $NMH$  and  $NML$ .


$$g = \frac{-2}{0.05 + 0.08} \left( \frac{1}{2.9 - 0.7} + \frac{1}{5 - 2.9 - 0.5} \right) = -16.6$$

$$V_{IL} = 2.9 + \frac{5 - 2.9}{-16.6} = 2.77 V$$

$$V_{IH} = 2.9 - \frac{2.9}{-16.6} = 3.1 V$$


$$NMH = 5 - 3.1 = 1.9 V$$

$$NML = 2.77 - 0 = 2.77 V$$

 

## Dynamic Behavior of CMOS Inverter

- ❑ Changing of the input doesn't instantaneously change the output of an inverter
- ❑ This is mostly due to the time it takes to charge or discharge the output/load capacitor
- ❑ It is important to know how long it takes to get the signal out of the inverter or any CMOS logic gate

 


ECE321 - Lecture 12

University of New Mexico

Slide: 11

## Definition: Propagation Delay

- ❑ Definition of propagation delay
  - is delay from where input crosses 50%Vdd to where output crosses 50%Vdd
  - Remember: the value of 50%Vdd is from switching threshold voltage ( $V_M$ )
  - $t_{pHL}$  is propagation delay when output switches from "High to Low"
  - $t_{pLH}$  is propagation delay when output switches from "Low to High"
- ❑ To compute delay, the inverter must be simplified

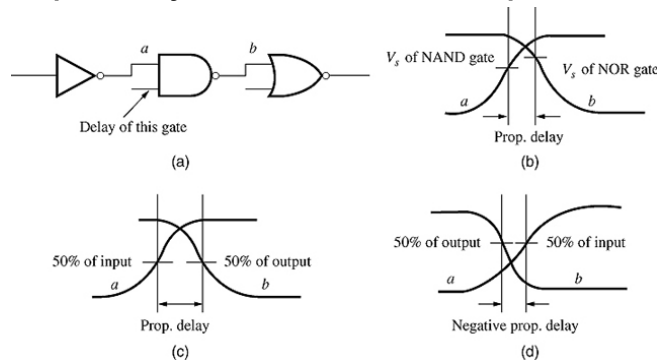


ECE321 - Lecture 12

University of New Mexico

Slide: 12

 
## Definition: 10%-90% Rise/Fall Times

- Definition of 10%-90% rise time
  - is delay from 10%V<sub>DD</sub> to 90%V<sub>DD</sub> in the output
  - $t_r$  is the rise time when output switches from “Low to High”
- Definition of 90%-10% fall time
  - is delay from 90%V<sub>DD</sub> to 10%V<sub>DD</sub> in the output
  - $t_f$  is the fall time when output switches from “High to Low”


 
## Definition: Linear Rise/Fall Times


- Definition of rise time (Hawkin's book)
  - is delay from 0 to V<sub>DD</sub> in the output assuming a constant current source model
  - $t_r$  is the rise time when output switches from “Low to High”
- Definition of fall time (Hawkin's book)
  - is delay from V<sub>DD</sub> to 0 in the output assuming a constant current source model
  - $t_f$  is the fall time when output switches from “High to Low”



## Delay Calculation in CMOS Inverter

- ❑ It is not easy to accurately calculate delay in CMOS inverter, because
  - CMOS inverter is a non-linear circuit, therefore exact delay calculation requires solving a non-linear differential equation
  - Most of the elements in the circuit is voltage dependent (transistor drive current, parasitic capacitances, channel length modulation, etc.)
- ❑ A simplified model is required for basic calculations and design process
- ❑ Note that SPICE actually does solve the non-linear circuit accurately, but is only good for final verification, not the design
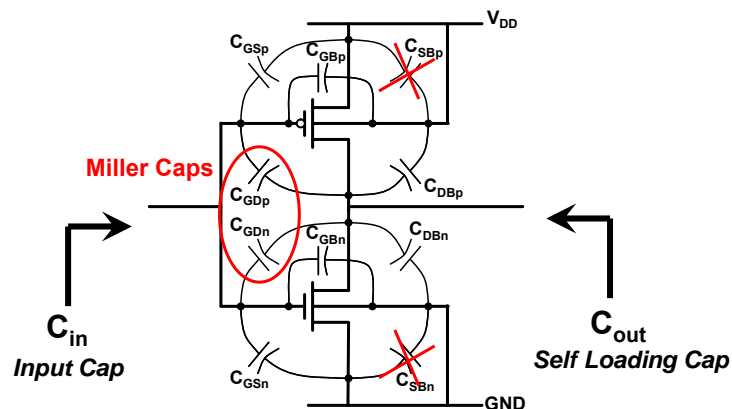
## Gate Input/Output Capacitances Components





$$C_{in} = (C_{GDp} + C_{GSp} + C_{GBp}) + (C_{GDn} + C_{GSn} + C_{GBn})$$

$$C_{out} = (2C_{GDp} + C_{DBp}) + (2C_{GDn} + C_{DBn})$$




## Propagation Delay Model

  

$$Q = I \cdot \Delta t = C \cdot \Delta V$$

$$\Delta t = \frac{C \cdot \Delta V}{I}$$

 
- Propagation delay is defined as the time between the input reaching  $V_{DD}/2$  and the output reaching  $V_{DD}/2$
- To simplify the model, let's assume  $I$  is a constant  $I_{av}$



$$t_{pLH} = t_2 - t_1 = \frac{C_L \cdot (V_{DD}/2)}{I_{av}}$$

## Propagation Delay Model

- How to compute  $I_{av}$  ?
  - Assume step input
  - NMOS goes into cutoff and stays there
  - PMOS goes into saturation at first because  $|V_{DS}| > |V_{GS}| - |V_T|$
  - PMOS will transition to linear, however, before  $V_{out}$  reaches  $V_{DD}/2$

 

$$I_{av} = \frac{I_{DS}(V_{out} = 0) + I_{DS}(V_{out} = V_{DD}/2)}{2}$$

$$I_{av} = \left(\frac{K'_p}{2}\right) \left(\frac{W_p}{L_p}\right) \left( \frac{(V_{DD} - |V_{tp}|)^2}{2} + \frac{V_{DD}(V_{DD} - |V_{tp}|)}{2} - \frac{V_{DD}^2}{8} \right)$$

## **Propagation Delay Model**

- A simpler model for  $I_{av}$  can be obtained by assuming that the PMOS stays in saturation the whole time, therefore acts as an ideal current source

$$I_{av} = \left(\frac{K'_p}{2}\right) \left(\frac{W_p}{L_p}\right) (V_{DD} - |V_{tp}|)^2$$

$$t_{pLH} = t_2 - t_1 = \frac{C_L \cdot (V_{DD}/2)}{I_{av}} \Rightarrow t_{pLH} = \frac{C_L \cdot V_{DD}}{K'_p \left(\frac{W_p}{L_p}\right) (V_{DD} - |V_{tp}|)^2}$$

- Assuming  $V_{DD} \gg V_{Tp}$

$$t_{pLH} = \frac{C_L}{K'_p \left(\frac{W_p}{L_p}\right) V_{DD}}$$

- Same arguments hold for  $t_{pHL}$

## **Minimum Delay Design Techniques**

- Reduce  $C_{in}$  and  $C_{out}$  – Careful layout, keep drain diffusion area as small as possible
- Reduce wiring capacitance – Careful layout, keep devices as close as possible
- Increase (W/L) of devices – Need to be careful not to get into self-loading effect
- Increase  $V_{DD}$  – Need to be careful not to get into  $V_{DSAT}$  or velocity saturation

## Example: CMOS Inverter Delay

- A CMOS inverter has  $V_{DD}=5V$  is designed such that  $(W/L)_n=10$  and  $(W/L)_p=20$ . Assume that  $V_{Tn}=0.7$ ,  $V_{Tp}=-0.6$ ,  $K'_n=100 \mu A/V^2$ ,  $K'_p=60 \mu A/V^2$ , and the load capacitance is 100fF.

1) Use  $I_{av}$  model to find  $t_{pHL}$ ,  $t_{pLH}$ ,  $t_{r(10\%-90\%)}$ , and  $t_{f(90\%-10\%)}$ .

2) Use constant current source model to find  $t_{pHL}$ ,  $t_{pLH}$ ,  $t_{r(10\%-90\%)}$ ,  $t_{f(90\%-10\%)}$ ,  $t_r$ , and  $t_f$ .

- *Answers:*

1)  $t_{pHL}=29.64 \text{ ps}$ ,  $t_{pLH}=23.73 \text{ ps}$ ,  $t_{r(10\%-90\%)=56.71 \text{ ps}$ , and  $t_{f(90\%-10\%)=70.98 \text{ ps}$

2)  $t_{pHL}=27.04 \text{ ps}$ ,  $t_{pLH}=21.52 \text{ ps}$ ,  $t_{r(10\%-90\%)=34.43 \text{ ps}$ , and  $t_{f(90\%-10\%)=43.27 \text{ ps}$ ,  $t_r=43.04 \text{ ps}$  and  $t_f=54.98 \text{ ps}$ .