

# ECE321 – Electronics I

## Lecture 13: CMOS Inverter: Dynamic Power

---

**Payman Zarkesh-Ha**

*Office: ECE Bldg. 230B*

*Office hours: Tuesday 2:00-3:00PM or by appointment*

*E-mail: [payman@ece.unm.edu](mailto:payman@ece.unm.edu)*

## *Review of Last Lecture*


---

- Propagation Delay
- Rise and Fall Times
- Input and Self Loading (Load) Capacitances
- Delay Approximation

## Today's Lecture

- Mostly Review of Lecture 2 for Dynamic Power Calculation

## CMOS Dynamic Power Consumption

 

$$\text{Energy/transition} = C_L * V_{dd}^2$$

$$\text{Power} = \text{Energy/transition} * f = C_L * V_{dd}^2 * f$$

$$P_d = \frac{1}{T} \int_0^T i_{VDD}(t) \cdot V_{DD} dt = \frac{V_{DD}}{T} \int_0^T C_L \frac{dV_{out}}{dt} dt = \frac{C_L V_{DD}}{T} \int_0^{V_{DD}} dV_{out} = \frac{C_L V_{DD}^2}{T} = C_L V_{DD}^2 f$$

- Need to reduce  $C_L$ ,  $V_{DD}$ , or  $f$  to reduce power

## Computing Active Power


- For clock circuit that toggles twice in each period (low-to-high and high-to-low), the active power consumption is computed as:

$$P_{active} = C_L V_{DD}^2 f$$

- For non-clock circuits that toggles occasionally (with probability of  $\alpha$ ) once in each period, the active power consumption is computed as:

$$P_{active} = \frac{1}{2} \alpha C_L V_{DD}^2 f = \frac{1}{2} (\alpha_{0 \rightarrow 1} + \alpha_{1 \rightarrow 0}) C_L V_{DD}^2 f$$
 
## Example: Active Power in a Clock Driver



*In this circuit, compute the power consumption in the inverter.*

**Answer: 2.17 W**

## ***Minimum Power Design Techniques***

---

- Prime choice: Reduce voltage!**
  - Recent years have seen an acceleration in supply voltage reduction
  - Design at very low voltages still open question (0.6 ... 0.9 V by 2015!)
- Reduce switching activity**
- Reduce physical capacitance**
- Reduce clock frequency, but use multi-core architecture to enhance performance**