

ECE321 – Electronics I

Lecture 16: Gate Sizing (Inverter Chain)

Payman Zarkesh-Ha

Office: ECE Bldg. 230B

Office hours: Tuesday 2:00-3:00PM or by appointment

E-mail: payman@ece.unm.edu

Review of Last Lecture


- Leakage Current and Power

Today's Lecture

- Gate Sizing (Inverter Chain)


Sizing Logic Path for Speed

 - Frequently, input capacitance of a logic path is constrained
- Logic also has to drive some capacitance
 - Example: output pad capacitive load is in the order of 10pF
- How do we size the inverter chain to achieve maximum speed?



- Wide gate to drive a large load must be driven in turn
 - Large block inputs “push their load into the chip”

Inverter Chain

 


$$C_i = \alpha^{i-1} C_{in} \quad i = 1, 2, \dots, n \quad \Rightarrow \quad C_L = \alpha^n C_{in}$$

$$\alpha^n = \frac{C_L}{C_{in}} \quad \Rightarrow \quad n = \frac{\ln\left(\frac{C_L}{C_{in}}\right)}{\ln \alpha}$$

$$t_{di} = \alpha \tau_0 \quad i = 1, 2, \dots, n \quad \Rightarrow \quad t_d = \sum_{i=1}^n t_{di} = n \alpha \tau_0 \quad \Rightarrow \quad t_d = \ln\left(\frac{C_L}{C_{in}}\right) \frac{\alpha}{\ln \alpha} \tau_0$$

Optimization Results

 

$$\alpha_{opt} = e \approx 2.7 \quad \Rightarrow \quad n_{opt} = \ln\left(\frac{C_L}{C_{in}}\right)$$

$$t_d = \sum_{i=1}^n t_{di} = n \alpha \tau_0$$

Example 1: Optimum Inverter Chain

An IC with a tapered buffer drives a load capacitance on a board that is 100 pF. The input capacitance of the logic gate originating the signal is 100 fF, and that gate has $W/L = 4$.

(a) How many buffer gates are required to optimally drive that load using the fixed tapered buffer model?

Answer:

$$n = 6.9$$

Seven total stages are needed. We must insert five tapered stages between the original gate and the output driver.

(b) Write the equation that predicts the W/L ratio of the final buffer in terms of the scaling factor and the originating gate W/L

(c) What is the W/L ratio of the final output buffer driver to the board?

Answer:

$$W/L = 1,614$$