

ECE321 – Electronics I

Lecture 28: DRAM & Flash Memories

Payman Zarkesh-Ha

Office: ECE Bldg. 230B

Office hours: Tuesday 2:00-3:00PM or by appointment

E-mail: payman@ece.unm.edu

Review of Last Lecture

Static Random-Access Memory (SRAM)


- SRAM cell
- SRAM architecture
- Sense amplifier

Today's Lecture

- Dynamic Random-Access Memory (DRAM)**
 - DRAM cells
 - DRAM Capacitor implementation
 - DRAM Sense amplifier
- Nonvolatile Memories**
 - EPROM
 - EEPROM
 - Flash

1T1R DRAM Cell

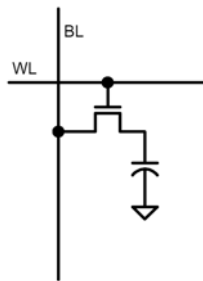- Stored bit is held dynamically on a capacitor**
- Very small storage cell – only 1 transistor**
 - Originally the capacitance was just the drain capacitance
- Unfortunately, charge doesn't scale – key to technology is packing more capacitance into a smaller area over time**
 - Two main approaches: (1) Trench capacitor, (2) stacked capacitor





DRAM Cell Observations

- ❑ 1T DRAM requires a sense amplifier for each bit line, due to charge redistribution read-out
- ❑ DRAM memory cells are single ended in contrast to SRAM cells
- ❑ The read-out of the 1T DRAM cell is destructive; read and refresh operations are necessary for correct operation
- ❑ When writing a “1” into a DRAM cell, a threshold voltage is lost. This charge loss can be circumvented by bootstrapping the word lines to a higher value than VDD



Sense Amplifier in DRAM

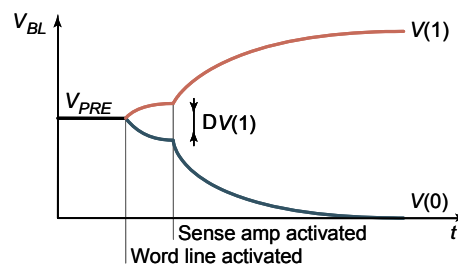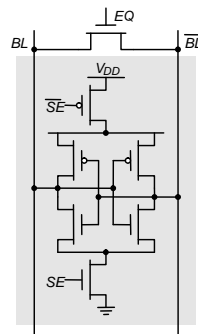- ❑ sense amp enabled with SE
- ❑ Initialized in its meta-stable point with EQ
- ❑ Once adequate voltage gap created, positive feedback quickly forces output to a stable operating point



DRAM Technology – Trench Capacitor

- ❑ Capacitor is the trench under select line
- ❑ The sidewalls and bottom of the trench are used for capacitor
- ❑ Trench is up to 5um deep

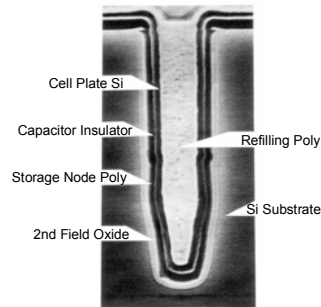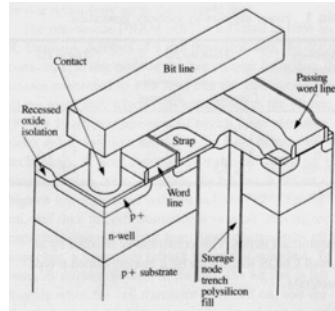




ECE321 - Lecture 28

University of New Mexico

Slide: 7

DRAM Technology – Stacked Capacitor

- ❑ Capacitor is above select transistor
- ❑ Polysilicon vias to polysilicon Plates

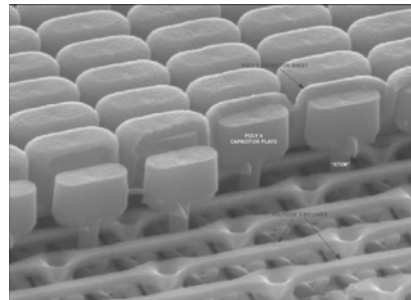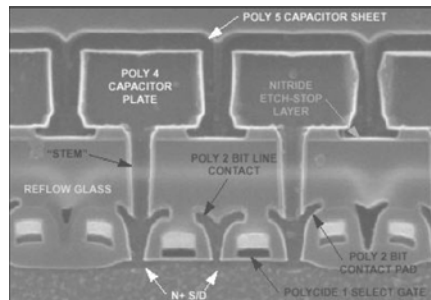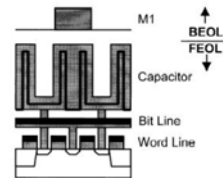


ECE321 - Lecture 28

University of New Mexico

Slide: 8

Semiconductor Memory Trends

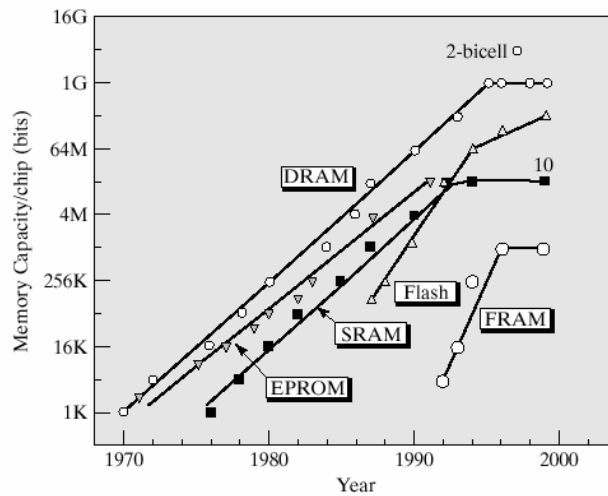


ECE321 - Lecture 28

University of New Mexico

Slide: 9

Nonvolatile Memories

- All present non-volatile memories are based on ROM memory configurations
 - All retain the single BL, although the sensing may be differential, using comparison to some reference voltage or replica BL
- The key to present memories is the ability to change the V_T of the transistor by adding or removing charge from a floating gate

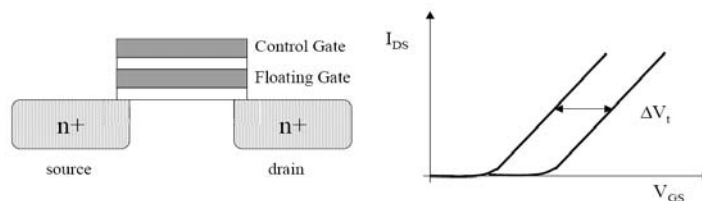


ECE321 - Lecture 28

University of New Mexico

Slide: 10


Erasable Programmable ROM (EPROM)

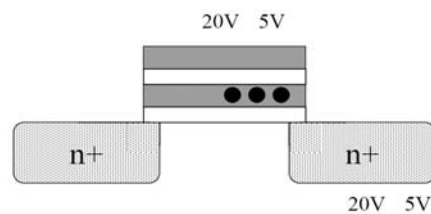- ❑ Uses the same ROM NOR topology but can electrically increase the V_T of a cell via hot electron injection to a floating gate
- ❑ Erase is by UV light: Energetic photons knock the charge off the floating gate
 - This is an off-line operation and requires expensive packages with windows
 - Windowless packages are used for one time program (OTP)



Electrically Erasable PROM (EEPROM)

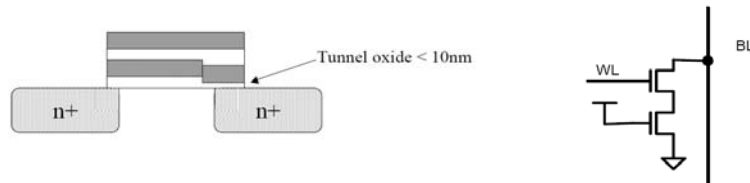- ❑ EEPROM allows electrical erase of the cells
 - By providing a thin oxide at the drain end, the proper voltage can remove the charge via Fowler-Nordheim tunneling
 - The cells require two transistors per cell however
- ❑ A drawback of this cell is V_T drift when exposed to read voltages. A separate access transistor helps to alleviate this problem, but at a significant density penalty



Flash Memories

- Flash memories also allow electrical erase but at better granularity and speed**
- A single thin oxide is used and a one transistor cell is possible**
- Flash is available in NOR and NAND varieties**
 - Flash is faster so can be main memory - still very slow compared to SRAM
 - It is impractical to directly run code from NAND so it is primarily popular as data storage, e.g., photos, USB drives, etc.
- Multiple level cells are possible with choices of 4 V_T s**
 - This requires multiple sense amplifiers or multiple passes
 - Programming precise values is difficult and “over-erase” must be avoided
- Scaling flash transistors is very difficult since the oxide cannot scale**
 - About 1 electron per month is the allowable loss