

ECE321 – Electronics I

Lecture 7: Basic Circuits with MOSFETs

Payman Zarkesh-Ha

Office: ECE Bldg. 230B

Office hours: Tuesday 2:00-3:00PM or by appointment

E-mail: payman@ece.unm.edu

Review of Last Lecture

- Threshold Voltage Equation

Today's Lecture


- Some Example of MOS Circuits

Example 1: Region of Operation

In the circuit configurations below:


- 1) Identify Drain and Source terminals assuming the device is an NMOS
- 2) Identify operating region of each transistor (cutoff, linear, saturation)
- 3) Write the drain current equation

Assume $V_T = 0.5 \text{ V}$, $K_n' \left(\frac{W}{L}\right) = 1 \frac{\text{mA}}{\text{V}^2}$. Ignore the body effect.

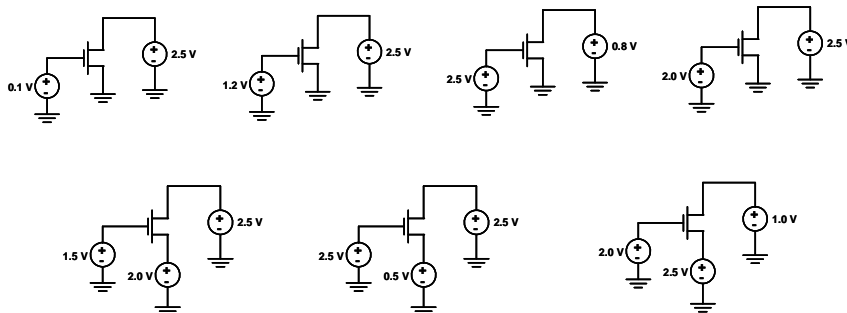


Example 2: Gate Bias Problem

- 3.7. Given that $K_n = 250 \mu\text{A}$, $V_{tn} = 0.5 \text{ V}$, and $W/L = 3$. What V_G makes transistor biased at the saturated/non-saturated boundary.

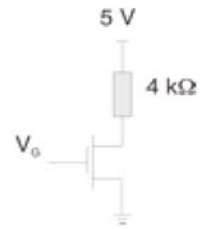

Example 3: PMOS Circuit

- 3.12. Calculate I_D and V_O for circuit where $V_{tp} = -0.8 \text{ V}$, $K_p = 30 \mu\text{A}/\text{V}^2$, and $W/L = 2$.

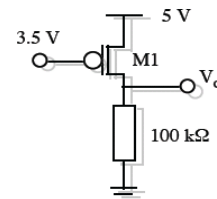

Example 4: Current Equation

- Find I_{in} as a function of V_{in} assuming $V_T < V_{in} < V_{DD} - V_T$ (assume long channel device and ignore channel length modulation)

