

its value for  $V_B = 0$  V? For what value of  $V_B$  is the transistor just at the edge of conduction? ( $v_{BE} = 0.5$  V) What values of  $V_E$  and  $V_C$  correspond? For what value of  $V_B$  does the transistor reach the edge of saturation? What values of  $V_C$  and  $V_E$  correspond? Find the value of  $V_B$  for which the transistor operates in saturation with a forced  $\beta$  of 2.

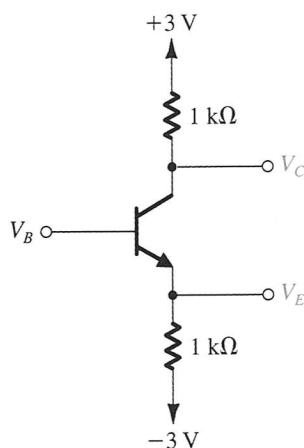


Figure P6.53

**6.54** For the transistor shown in Fig. P6.54, assume  $\alpha \simeq 1$  and  $v_{BE} = 0.5$  V at the edge of conduction. What are the values of  $V_E$  and  $V_C$  for  $V_B = 0$  V? For what value of  $V_B$  does the transistor cut off? Saturate? In each case, what values of  $V_E$  and  $V_C$  result?

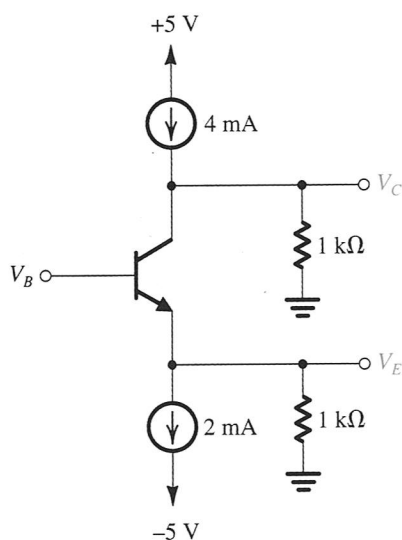


Figure P6.54

**D 6.55** Consider the circuit in Fig. P6.51 with the base voltage  $V_B$  obtained using a voltage divider across the 3-V supply. Assuming the transistor  $\beta$  to be very large (i.e., ignoring the base current), design the voltage divider to obtain  $V_B = 1.2$  V. Design for a 0.1-mA current in the voltage divider. Now, if the BJT  $\beta = 100$ , analyze the circuit to determine the collector current and the collector voltage.

**6.56** A single measurement indicates the emitter voltage of the transistor in the circuit of Fig. P5.56 to be 1.0 V. Under the assumption that  $|V_{BE}| = 0.7$  V, what are  $V_B$ ,  $I_B$ ,  $I_E$ ,  $I_C$ ,  $V_C$ ,  $\beta$ , and  $\alpha$ ? (Note: Isn't it surprising what a little measurement can lead to?)

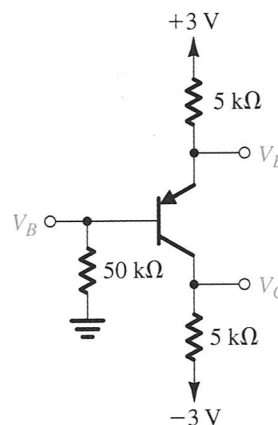


Figure P6.56

**D 6.57** Design a circuit using a *pn*p transistor for which  $\alpha \simeq 1$  using two resistors connected appropriately to  $\pm 3$  V so that  $I_E = 0.5$  mA and  $V_{BC} = 1$  V. What exact values of  $R_E$  and  $R_C$  would be needed? Now, consult a table of standard 5% resistor values (e.g., that provided in Appendix J) to select suitable practical values. What values of resistors have you chosen? What are the values of  $I_E$  and  $V_{BC}$  that result?

**6.58** In the circuit shown in Fig. P6.58, the transistor has  $\beta = 40$ . Find the values of  $V_B$ ,  $V_E$ , and  $V_C$ . If  $R_B$  is raised to 100 kΩ, what voltages result? With  $R_B = 100$  kΩ, what value of  $\beta$  would return the voltages to the values first calculated?

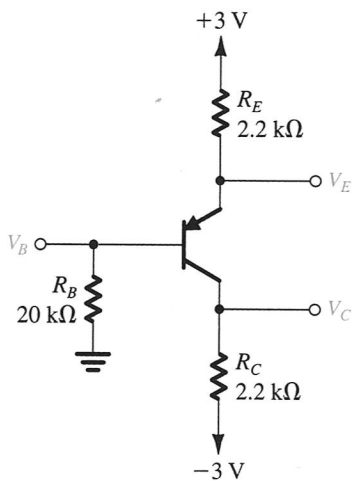


Figure P6.58

**6.59** In the circuit shown in Fig. P6.58, the transistor has  $\beta = 50$ . Find the values of  $V_B$ ,  $V_E$ , and  $V_C$ , and verify that the transistor is operating in the active mode. What is the largest value that  $R_C$  can have while the transistor remains in the active mode?

**SIM 6.60** For the circuit in Fig. P6.60, find  $V_B$ ,  $V_E$ , and  $V_C$  for  $R_B = 100 \text{ k}\Omega$ ,  $10 \text{ k}\Omega$ , and  $1 \text{ k}\Omega$ . Let  $\beta = 100$ .

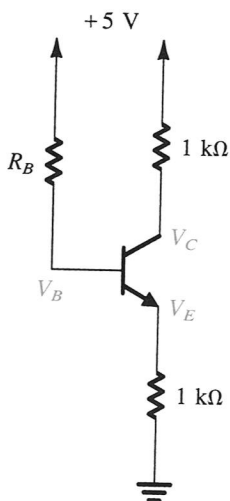


Figure P6.60

**6.61** For the circuits in Fig. P6.61, find values for the labeled node voltages and branch currents. Assume  $\beta$  to be very high.

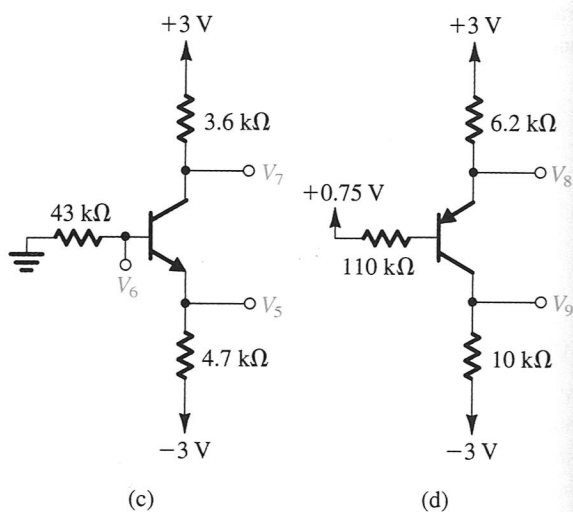
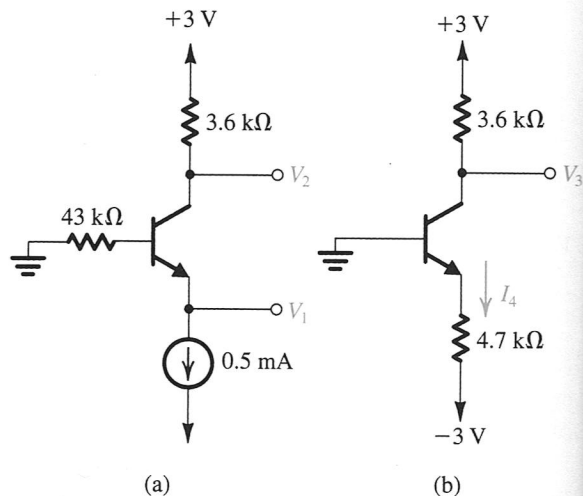


Figure P6.61

**SIM** = Multisim/PSpice; \* = difficult problem; \*\* = more difficult; \*\*\* = very challenging; D = design problem

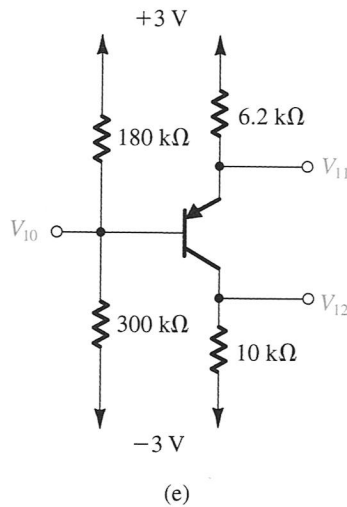


Figure P6.61 continued

**\*6.62** Repeat the analysis of the circuits in Problem 6.61 using  $\beta = 100$ . Find all the labeled node voltages and branch currents.

**D \*\*6.63** It is required to design the circuit in Fig. P6.63 so that a current of 1 mA is established in the emitter and a voltage of  $-1$  V appears at the collector. The transistor type used has a nominal  $\beta$  of 100. However, the  $\beta$  value can be as low as 50 and as high as 150. Your design should ensure that the specified emitter current is obtained when  $\beta = 100$  and that at the extreme values of  $\beta$  the emitter current does not change by more than 10% of its nominal value. Also, design for as large a value for  $R_B$  as possible. Give the values of  $R_B$ ,  $R_E$ , and  $R_C$  to the nearest kilohm. What is the expected range of collector current and collector voltage corresponding to the full range of  $\beta$  values?

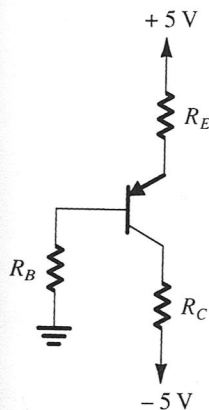


Figure P6.63

**D 6.64** The pnp transistor in the circuit of Fig. P6.64 has  $\beta = 50$ . Find the value for  $R_C$  to obtain  $V_C = +2$  V. What happens if the transistor is replaced with another having  $\beta = 100$ ? Give the value of  $V_C$  in the latter case.

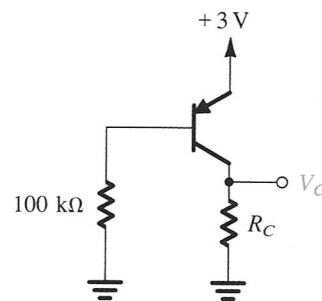


Figure P6.64

**\*\*\*6.65** Consider the circuit shown in Fig. P6.65. It resembles that in Fig. 6.30 but includes other features. First, note diodes  $D_1$  and  $D_2$  are included to make design (and analysis) easier and to provide temperature compensation for the emitter-base voltages of  $Q_1$  and  $Q_2$ . Second, note resistor  $R$ , whose purpose is to provide negative feedback (more on this later in the book!). Using  $|V_{BE}|$  and  $V_D = 0.7$  V independent of current, and  $\beta = \infty$ , find the voltages  $V_{B1}$ ,  $V_{E1}$ ,  $V_{C1}$ ,  $V_{B2}$ ,  $V_{E2}$ , and  $V_{C2}$ , initially with  $R$  open-circuited and then with  $R$  connected. Repeat for  $\beta = 100$ , with  $R$  open-circuited initially, then connected.

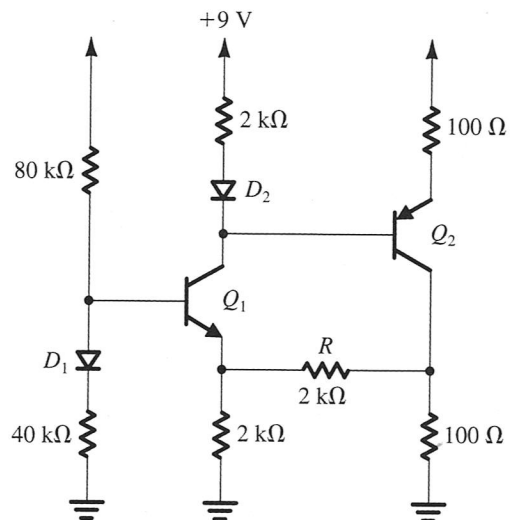


Figure P6.65

\*6.66 For the circuit shown in Fig. P6.66, find the labeled node voltages for:

- (a)  $\beta = \infty$   
 (b)  $\beta = 100$

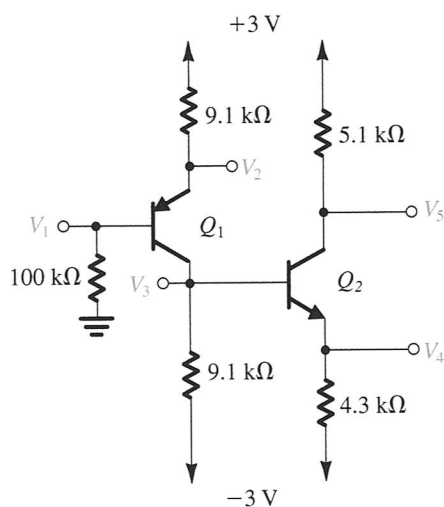


Figure P6.66

D \*6.67 Using  $\beta = \infty$ , design the circuit shown in Fig. P6.67 so that the emitter currents of  $Q_1$ ,  $Q_2$ , and  $Q_3$

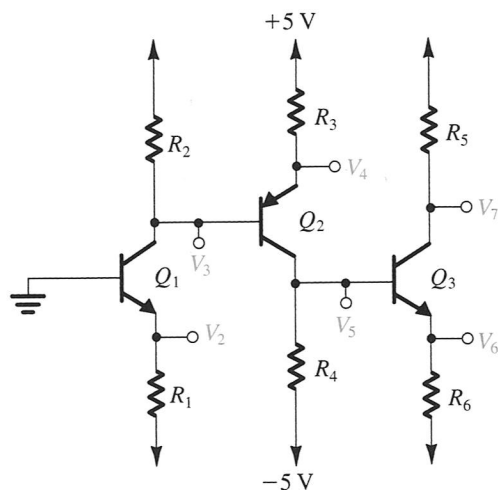


Figure P6.67

are 0.5 mA, 0.5 mA, and 1 mA, respectively, and  $V_3 = 0$ ,  $V_5 = -2$  V, and  $V_7 = 1$  V. For each resistor, select the nearest standard value utilizing the table of standard values for 5% resistors in Appendix J. Now, for  $\beta = 100$ , find the values of  $V_3$ ,  $V_4$ ,  $V_5$ ,  $V_6$ , and  $V_7$ .

\*6.68 For the circuit in Fig. P6.68, find  $V_B$  and  $V_E$  for  $v_i = 0$  V, +2 V, -2.5 V, and -5 V. The BJTs have  $\beta = 50$ .

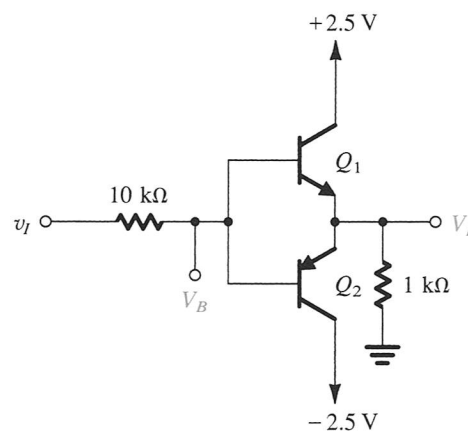


Figure P6.68

\*\*6.69 All the transistors in the circuits of Fig. P6.69 are specified to have a minimum  $\beta$  of 50. Find approximate values for the collector voltages and calculate forced  $\beta$  for each of the transistors. (Hint: Initially, assume all transistors are operating in saturation, and verify the assumption.)