

ECE321 – Electronics I

Lecture 17: Interconnect Modeling I

Payman Zarkesh-Ha

Office: ECE Bldg. 230B

Office hours: Tuesday 2:00-3:00PM or by appointment

E-mail: payman@ece.unm.edu

Review of Last Lecture

- Gate Sizing (Inverter Chain)

Today's Lecture

- Interconnect Resistance**
- Interconnect Capacitance**
- Interconnect Inductance**

Interconnect Modeling


- Interconnect parasitics**
 - reduce reliability (crosstalk noise)
 - affect performance and power consumption
- Interconnect Modeling**
 - Parasitic Capacitance
 - Parasitic Resistance
 - Parasitic Inductance

Example: Intel 0.25um backend process

5 metal layers
Ti/Al - Cu/Ti/TiN
Polysilicon dielectric


LAYER	PITCH	THICK	A.R.
Isolation	0.67	0.40	-
Polysilicon	0.64	0.25	-
Metal 1	0.64	0.48	1.5
Metal 2	0.93	0.90	1.9
Metal 3	0.93	0.90	1.9
Metal 4	1.60	1.33	1.7
Metal 5	2.56	1.90	1.5
	μm	μm	

Layer pitch, thickness and aspect ratio

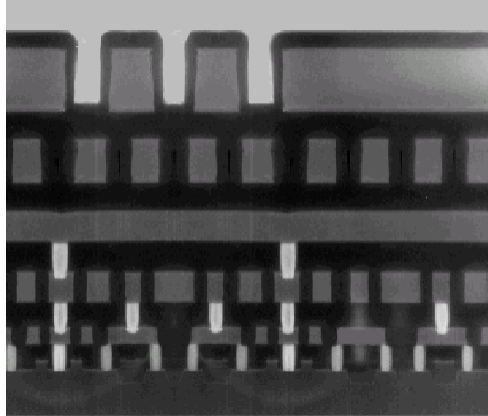

Interconnect Resistance

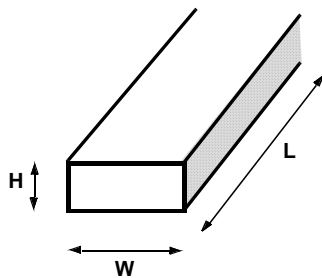- ❑ Extraction of interconnect capacitance is simpler except for special cases (test chips where accurate resistance of a pattern is needed)
- ❑ Sheet resistance is an easy method of resistance measurement in layout (Only the metal aspect ratio is needed, no thickness information)




$$R = \frac{\rho L}{WH}$$

$$R = \left(\frac{\rho}{H}\right) \frac{L}{W} = R_{\square} \frac{L}{W}$$

Sheet Resistance

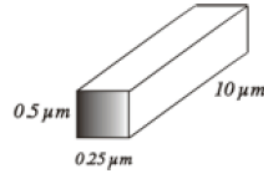Example: Interconnect Resistance

If the line is made of Cu, calculate the line resistance using sheet resistance at $T=20^{\circ}\text{C}$.



The sheet resistance is $R_{\text{square}} = \frac{\rho}{t} = \frac{1.72 \mu\Omega \cdot \text{cm}}{0.5 \mu\text{m}} \times \frac{10^4 \mu\text{m}}{\text{cm}} = \frac{33.99 \text{ m}\Omega}{\text{square}}$



And the total number of squares is $l/w = 10 \mu\text{m}/0.25 \mu\text{m} = 40$ squares. The total resistance is then

$$R = 33.99 \text{ m}\Omega \times 40 = 1.360 \Omega$$

You get the same result from Eq (1), but deal with one less constant in the sheet resistance calculation.


Sheet Resistance

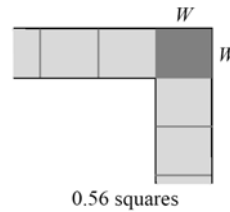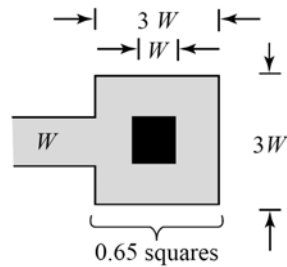- Measurement shows that the effective number of squares of the "dog bone" style contact region is 0.65 and for a 90° corner is 0.56




Interconnect Capacitance

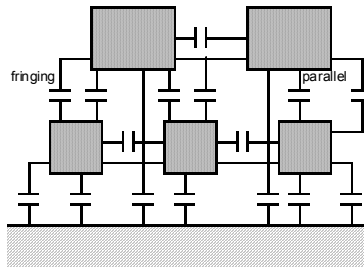- ❑ Extraction of interconnect capacitance in modern VLSI technology is very complicated because of
 - Non-homogenous dielectric (etch stop, barrier liner, etc.)
 - Complex pattern of neighboring interconnects (need 3D modeling)
- ❑ There are two types of capacitances:
 - Ground capacitances
 - Coupling capacitances



Interconnect Capacitance Modeling

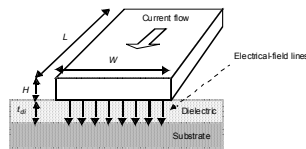
- ❑ Often simple parallel plate model is used for hand calculation



$$C_{int} = \frac{\epsilon_{di}}{t_{di}} WL$$

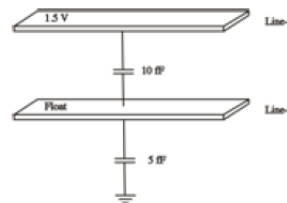Example:


Consider the static situation in the figure where line-1 is at 1.5 V and line-2 is floating. What is the induced voltage on line-2?



$$V_2 = \left[\frac{10}{10+5} \right] 1.5 \text{ V} = 1.0 \text{ V}$$

Interconnect Inductance

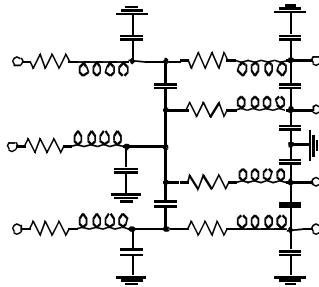- ❑ Extraction and modeling of interconnect inductance is extremely hard because of
 - Non-identified return path
 - Unlike capacitance, the effect of inductance goes beyond nearest neighbors
- ❑ It is used only for specific nets such as clock and power supply interconnects
- ❑ Has not yet been used by industry for timing analysis



Example: Inductance in Power Supply

The inductance in a particular IC connecting metal is 200 pH. What is the inductive voltage generated during a current rise time of 10^9 A/s?

$$v_L = L \frac{di}{dt} = 200 \times 10^{-12} \times 10^9 = 200 \text{ mV}$$

Many ICs use power supply voltages on the order of 1.0 V and less. A 200 mV inductive bite is a severe temporary weakening of the normal voltage that drives logic circuitry.

Dealing with Interconnect Parasitics

- Reduce interconnect Capacitance**
 - Use better dielectric material (low-K dielectric)
 - Reduce wire-length (efficient layout)
 - Increase wire spacing
- Reduce Interconnect Resistance**
 - Use better conductor material (Copper)
 - Reduce wire-length (efficient layout)
 - Increase wire width
- Reduce Interconnect Inductance**
 - Use proper return path
 - Slow down the ramp time